

DC Machines

Motor

$P_m \rightarrow$ Motor

Generator

$P_e \rightarrow$ Generator

Motor

Generator

$P_e \rightarrow$ Motor

Generator


$P_m \rightarrow$ Generator

DC Generators

There are five major types of dc generators:

- 1) Separately excited dc generator ✓
- 2) Shunt (parallel) dc generator ✓
- 3) Series dc generator ✓
- 4) Cumulatively Compounded dc generator ✓
- 5) Differentially Compounded dc generator ✓

(factor 1/e static
reduces current)

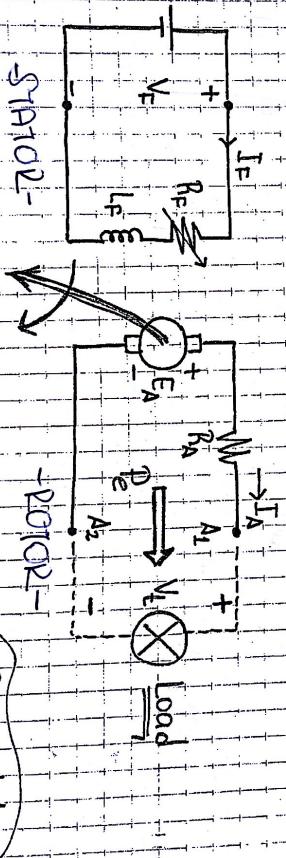


$$I_F = \frac{V_F}{R_F}$$

$$(E_A = V_t + R_A I_A)$$

Separately
Excited
generator

Shunt DC generator

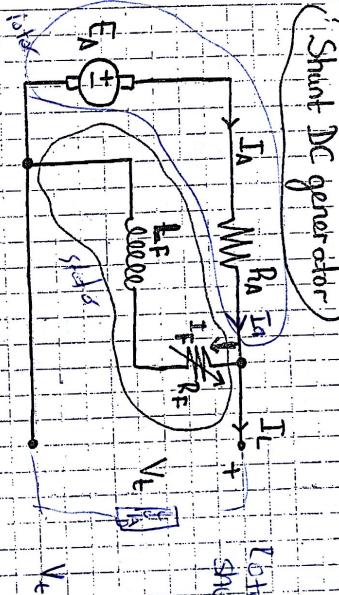Constante statore decreases
shunt coefficient




$$V_E = E_A - R_F I_F$$

$$= E_A - R_F I_F + R_F I_L$$

$$\begin{aligned} I_F &= \frac{V_E}{R_F} \\ E_A &= R_A I_A + V_E \\ I_A &= I_F + I_L \end{aligned}$$

Series DC Generator

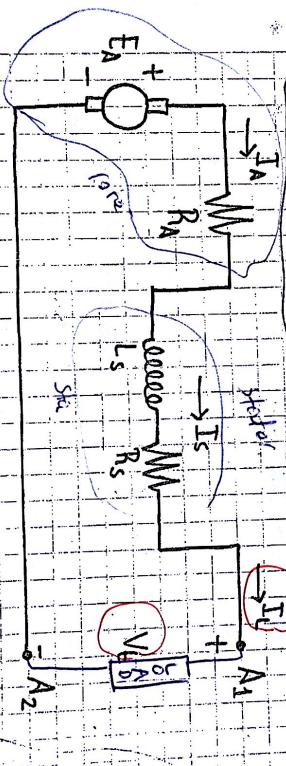all dolum uchukucu terminal voltage, decreasing I_L



$$\begin{aligned} I_A &= I_S = I_L \\ E_A &= (R_A + R_S) I_A + V_E \end{aligned}$$

$$\begin{cases} I_A = I_S = I_L \\ E_A = (R_A + R_S) I_A + V_E \end{cases}$$

Response yok alım artırua tencere
voltage, dekha kırıcı du inelte

26-a


29 Mart Salı 2014

DC Generators # (... konuya devam)

Cumulatively Compounded DC Generators

$$E_A = V_t + I_A(R_s + R_A)$$

$$I_A = I_L + I_F$$

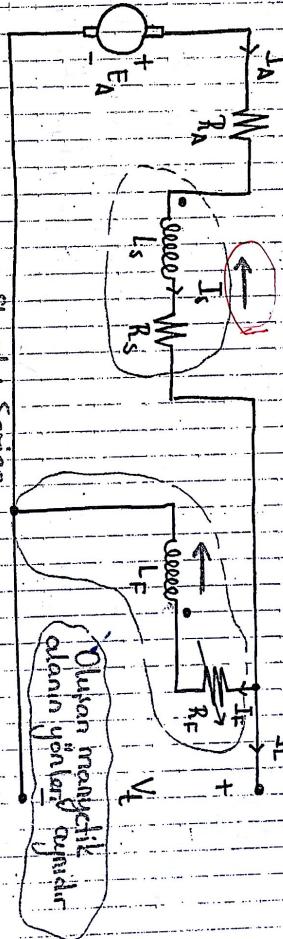


* In Compounded dc machines there are two field windings. One of them is series with the armature winding and the other is parallel.

Differentially Compounded DC Generators

Shunt + Series

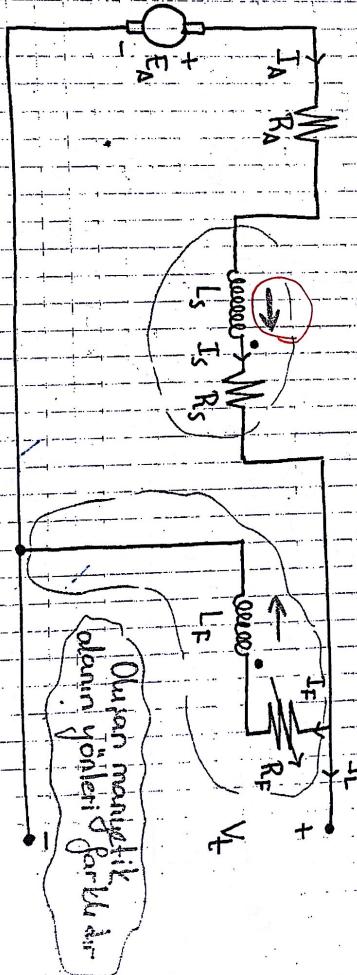
In Differentially Compounded DC Generators, there are two field windings. One of them is in series with the armature winding and the other is in parallel.



$$(E_A = V_t + I_A(R_s + R_A))$$

Oluşan manjistik alanın yönleri farklıdır

Parallel Connection of DC generators

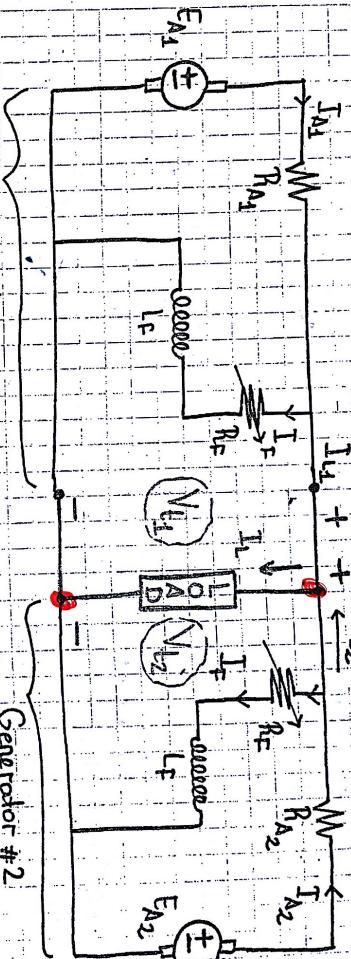

Generator #1

$I_L = I_1 + I_2$

Generator #2

$$P_L > P_{gen_1} \quad \text{OR} \quad P_L > P_{gen_2}$$

The requirements which are needed to connect two generator in parallel are as,


1. The voltage polarities of two generators should be same.
2. The voltage level of two generators should be approximately equal.

The Magnetization Curve of a DC Generator

constant field flux
magnetic circuit

constant field flux
magnetic circuit



constant field flux
magnetic circuit

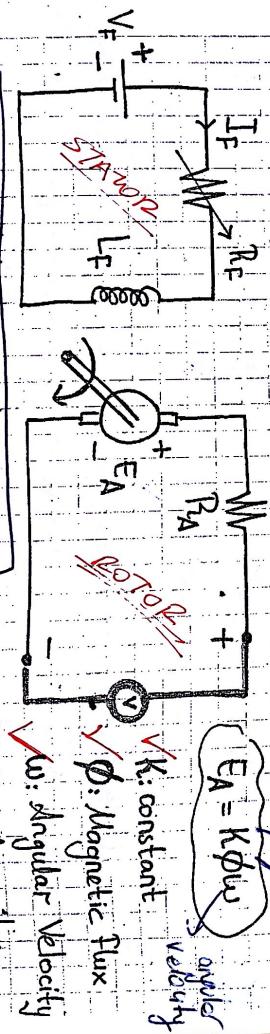

$$\frac{E_A}{E_{AV}} = \frac{K\Phi_1 w_1}{K\Phi_2 w_2} = \frac{\Phi_1}{\Phi_2} \times \frac{w_1}{w_2}$$

K: constant
w: angular velocity
of armature
(rad/sec)

$$E_A = \epsilon \phi W$$

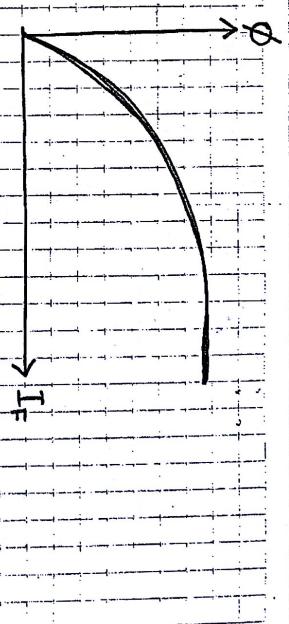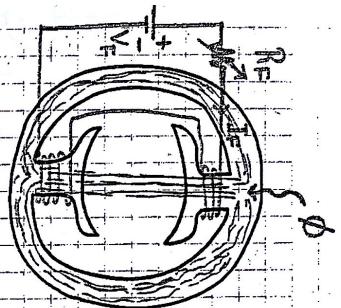

Since $E_A \propto \phi \Rightarrow$ The relationship between "E_A and I_F" is similar to that of "φ and I_F".

(for a constant speed) ✓



Example: A separately excited dc generator is rated at 172 kW, 430V, 400A and 1800 r/min. The magnetization curve is shown below. The machine has the following characteristics:

Rating parameters

$$R_A = 0.05 \Omega \checkmark$$

$$R_F = 20 \Omega \checkmark$$

$$R_{adj} = 0 \text{ to } 300 \Omega \checkmark$$


$$V_F = 430V$$

$$N_F = 1000 \text{ turns/pole}$$

✓ turns number of field windings

- a) If the variable resistance, R_{adj}, in the generator's field circuit is adjusted to 63 Ω and the generator's prime mover is driving it at 1600 r/min, what is the generator's no-load terminal voltage?

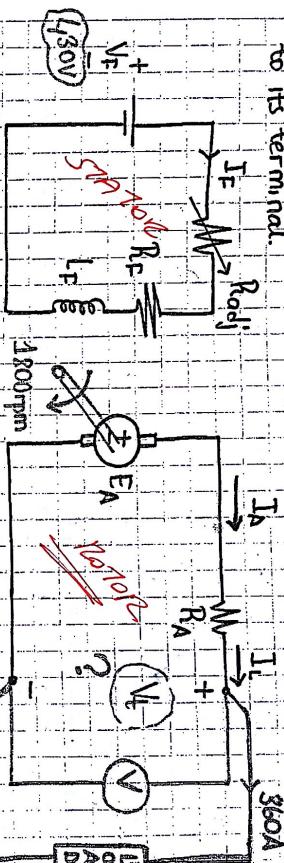b) What would its voltage be if a 360-A load were connected to its terminal.



Solution:



$$a) I_F = \frac{E_A}{R_F + R_{Adi}} = \frac{430}{20 + 63} = 5.2 \text{ A} \quad \checkmark$$

E_A at 1800 rpm $\Rightarrow 430$
 E_A at 1600 rpm $\Rightarrow ?$

$$\rightarrow E_A = K\phi\omega \quad (\text{rad/sec})$$

$$\begin{cases} E_{A1} = K\phi_1\omega_1 \\ E_{A2} = K\phi_2\omega_2 \end{cases} \Rightarrow \frac{E_{A1}}{E_{A2}} = \frac{K\phi_1\omega_1}{K\phi_2\omega_2} = \frac{\phi_1}{\phi_2} \times \frac{\omega_1}{\omega_2}$$

1800 rpm → nominal value

28-a

$$(E_A \text{ at } 1600 \text{ rpm}) \Rightarrow 450 \times \frac{1600}{1800} = \underline{\underline{382V}}$$

b) For load current of 360 A, find the terminal voltage V_t .

$$E_A = V_t + R_A I_A$$

$$382 = V_t + 0.05 \times 360$$

$$V_t = 382 - 18 = \underline{\underline{364V}}$$

30 March 2014 - CSE

DC Generators:
⇒ Relationship between terminal voltage and load current


Shunt DC generator



Series DC Generator




Compulsively Compounded DC generator

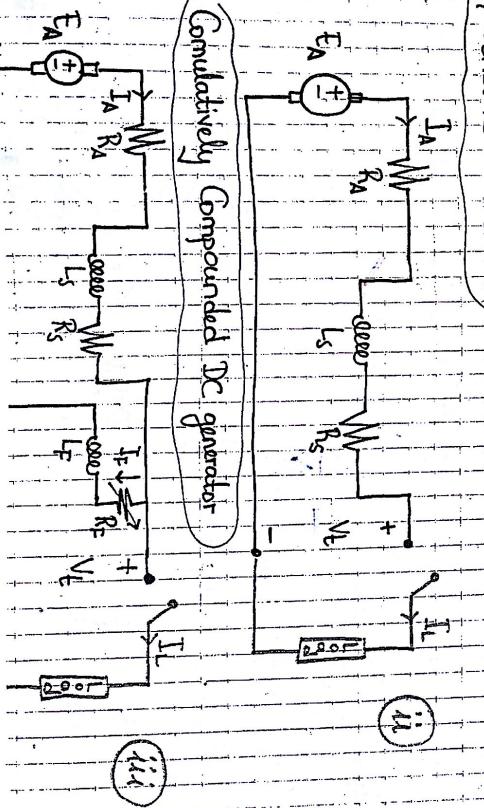

$$\text{i) } I_A = I_F + I_L \quad \checkmark$$
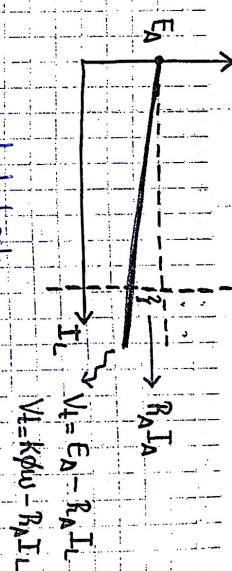
$$\left\{ \begin{array}{l} V_t = E_A - R_A I_A \quad \checkmark \\ V_t = K\phi\omega - R_A I_A \end{array} \right.$$



$$\text{ii) } I_A = I_L$$

$$\left\{ \begin{array}{l} V_t = E_A - (R_A + R_S) I_A \quad \checkmark \\ V_t = [E_A - K\phi\omega] - (R_A + R_S) I_A \end{array} \right.$$


$$\left\{ \begin{array}{l} V_t = K\phi\omega - (R_A + R_S) I_A \end{array} \right.$$

parallel load

$$\text{iii) } I_A = I_F + I_L$$

$$\left\{ \begin{array}{l} V_t = E_A - (R_A + R_S) I_A \quad \checkmark \\ V_t = [E_A - K\phi\omega] - (R_A + R_S) I_A \end{array} \right.$$
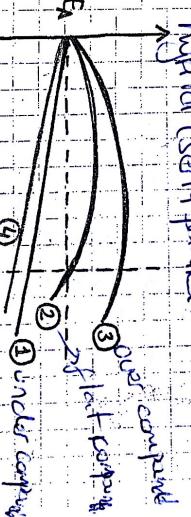
$$\left\{ \begin{array}{l} V_t = K\phi\omega - (R_A + R_S) I_A \end{array} \right.$$



- i) \Rightarrow The output voltage of a shunt DC generator decreases with increasing in "Load Current".

- ① Under Compounded
② flat Compounded
③ Over Compounded
④ Shunt

* In DC generators: The output voltage can be controlled.

1. Varying the field current.
2. Varying the speed of rotation.

Power Flow and Losses in DC Machines

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{P_{in} - \sum \text{Losses}}{P_{in}} \times 100$$

Losses

- ✓ 1- Electrical or Copper Losses (R_I^2)
- ✓ 2- Brush Loss
- ✓ 3- Core Loss
- ✓ 4- Mechanical Loss
- ✓ 5- Stray load loss

1 Electrical or Copper Losses

$$P_{BD} = R_A I_A^2 + R_F I_F^2$$

loss of armature
winding

loss of field winding

2 Brush Loss

$$P_{BD} = V_{BD} I_A$$

with brushes

P_{BD} : Brush power loss ✓

V_{BD} : Brush voltage drop ✓

I_A : Armature resistance ✓

3- Core Loss

- a- Hysteresis Loss
- b- Eddy-Current Loss

4- Mechanical loss

a - Frictional loss (sur Name kaupiyan)

b - Windage loss (air dara rojka deng koy)

5. Stray load loss

Automobile huppi

: the losses can not be placed in one of the previous categories

⇒ It is about 1% of full load


for Generators;

$$P_{conv}$$

$$P_{out} = V_t I_t \omega$$

For Motors,

$$P_{conv}$$

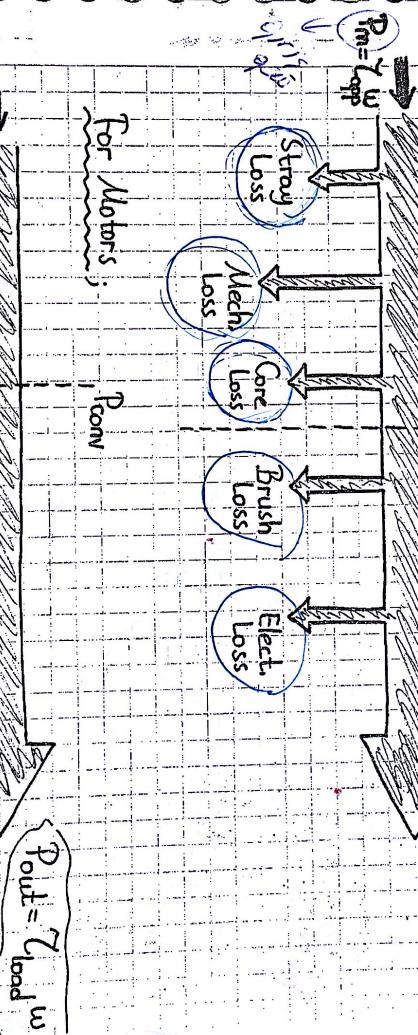

* Power Flow Diagram for

Generators and Motors

30-a

31 Mart 2014 Perşembe

$\Rightarrow \phi'$ nin genişliği "önemli değildir", değişimini "önemlidir!"

Quiz #1

Şoru #2:


Faraday Yasası

e

e

e

N

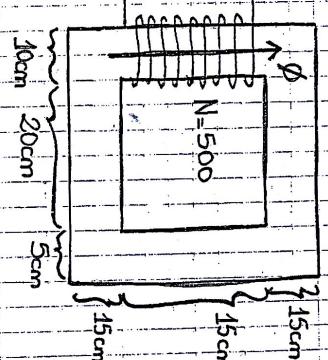

$$\Rightarrow \phi = \text{Constant} = 100 \text{ Web}$$

$$e \rightarrow \frac{d\phi}{dt} = 0$$



$$0 \leq t \leq 2 \rightarrow e = 500 \times \frac{d\phi}{dt} = 500 \times \frac{1 \times 10^{-2} - 0}{2 \times 10^{-3}} = \frac{2500}{7} \text{ V}$$

$$2 \leq t \leq 5 \rightarrow e = 500 \times \frac{-0.01 - 0.01}{3 \times 10^{-3}} = \frac{-2 \times 10^{-2} \times 500}{3 \times 10^{-3}} = \frac{-3333}{7} \text{ V}$$

$$-5 \leq t \leq 7 \rightarrow e = 500x \frac{0 - (-0.01)}{2 \times 10^{-3}} = 2500V$$

$$7 \leq t \leq 8 \rightarrow e = 500x \frac{0.01 - 0}{1 \times 10^{-3}} = 5000V$$

Example:

Draw the waveform of "e" considering B given in the below


(yanındaki sorunun ϕ grafiği, bu soruda artı B (kaldırma))

ϕ grafiğin birimleri 200 ile -200 arasında olur.

figure shown

$$\phi = A_1 \cdot B_1 = A_2 \cdot B_2$$
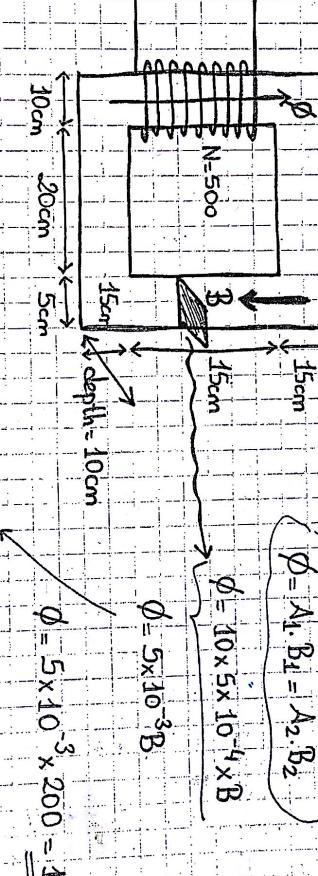
$$\phi = 10 \times 5 \times 10^{-4} \times B$$




$$= 1$$

3 den ϕ hesabi yapıldığında ϕ 'nın grafiğinde aynı cikar sadece

(max-min) sınırları değişir $\rightarrow (1, -1)$

$\uparrow \phi(\text{weber})$

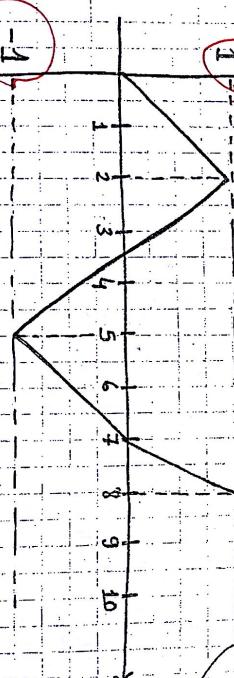ϕ nüvenin her yerinde aynıdır, B ise değişkeni olan kırın değişikliğinden dolayı...



31-a

Soru #1:

For a 2000 VA, 230/115 transformer;

$$V_{oc} = 230V$$

$$I_{oc} = 0.45A$$

$$P_{oc} = 30W$$

open circuit

$$V_{sc} = 13.2V$$

$$I_{sc} = 6A$$

$$P_{sc} = 20.1W$$

short circuit


r_{eq}, x_{eq}

a) equivalent circuit

b) for $P_f = 0.8$ lagging at rating conditions $V_R = ?$ ✓

c) for $P_f = 0.8$ lagging at rating conditions $\gamma = ?$

(use approximate equivalent circuit)

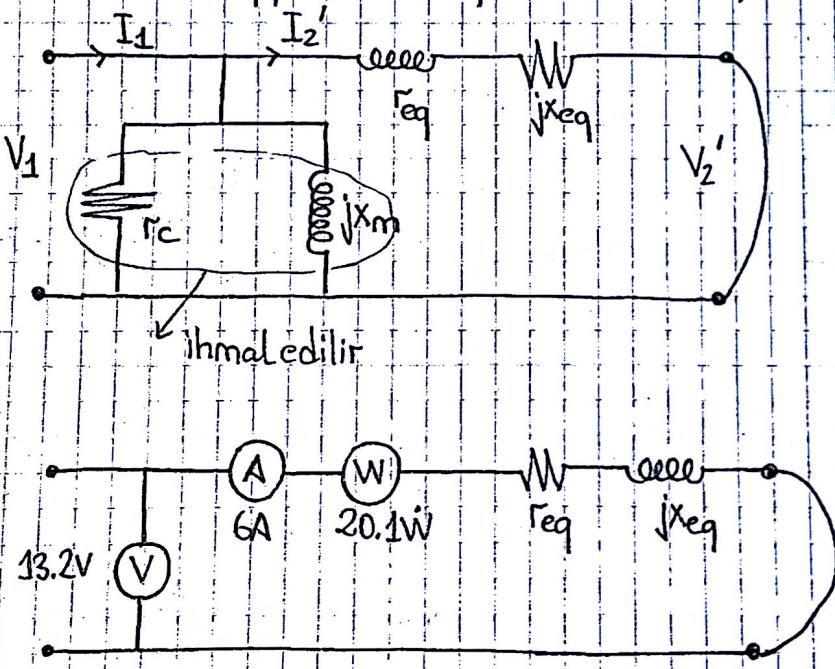

$$r_{eq} I_{sc}^2 = P_{sc}$$

$$* r_{eq} = \frac{20.1}{6^2}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{13.2}{6}$$

$$x_{eq} = \sqrt{Z_{sc}^2 - r_{eq}^2}$$

$\Rightarrow r$ and x_m are derived using the open circuit test results.

$$\cos \theta_{oc} = \frac{P_{oc}}{V_{oc} \times I_{oc}} = \frac{30}{230 \times 0.45}$$

$$\theta_{oc} = \cos^{-1} \frac{30}{230 \times 0.45}$$

$$I_{oc} \angle -\theta_{oc} = \frac{1}{r_c} + \frac{1}{jx_m}$$

$$V_{oc} \angle 0^\circ = \frac{1}{r_c} + \frac{1}{jx_m}$$

→ SIVAVUPAVAKADAR

DC Motors

1. Separately excited dc motors

2. Shunt dc motors

3. Series dc motors

4. Compounded dc motors

Note: Generators also apply


5. Permanent magnet dc motors

$$V_t = E_A + R_A I_A$$

$$I_L = I_A$$

$$V_t = E_A + K_A \omega$$

(1) Separately excited dc motors

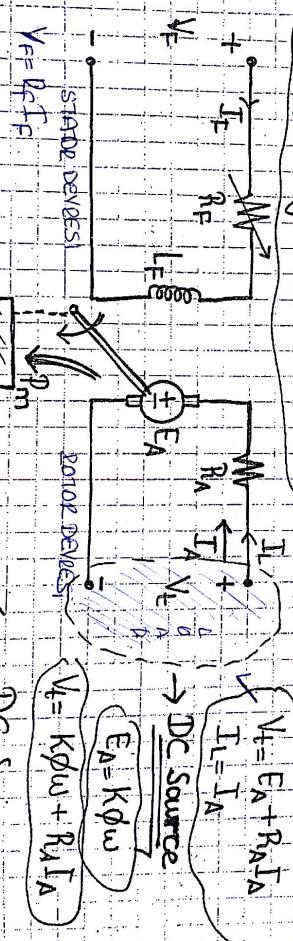


(There is needed for two separate DC Sources)



32-a

Sinai souls.

2. Shunt DC Motors

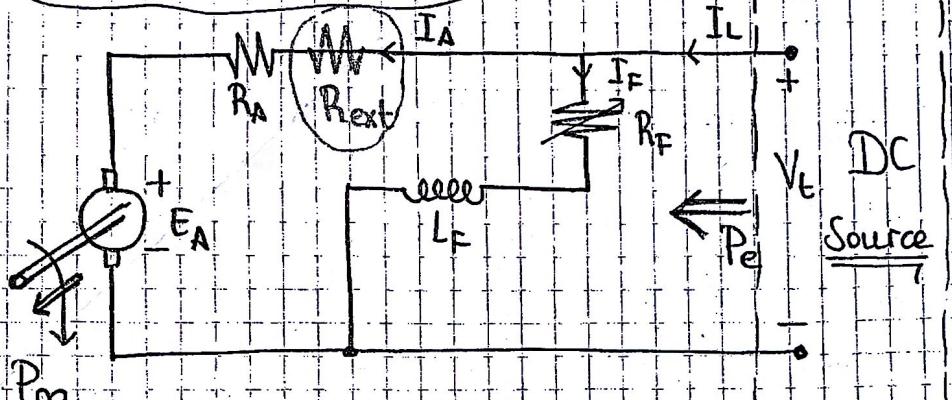

$$P_e = P_{in} = V_t I_L$$

$$P_{out} = P_m = \gamma_m \omega$$

Torque
(N.m.)

I_L = I_a + I_F / TORQUE-SPEED CHARACTERISTICS
OF SHUNT DC MOTOR

$$V_t = R_A I_A + E_A$$

$$\gamma = K \phi I_A$$

$$I_A = \frac{\gamma}{K \phi}$$

$$V_t = R_A \frac{\gamma}{K \phi} + K \phi \omega$$

$$K \phi \omega = V_t - R_A \frac{1}{K \phi} \gamma$$

$$\omega = \frac{1}{K \phi} V_t - \frac{R_A}{(K \phi)^2} \gamma$$

$$E_A = K \phi \omega$$

$$\gamma = K \phi I_A$$

* * * Armature current

magnetic field produced by field windings.


The relationship between torque and speed of a shunt dc motor

$$R_F ? \quad \phi = \frac{V_F}{R_F}$$

32-a

grav. solv.

2- Shunt DC Motors

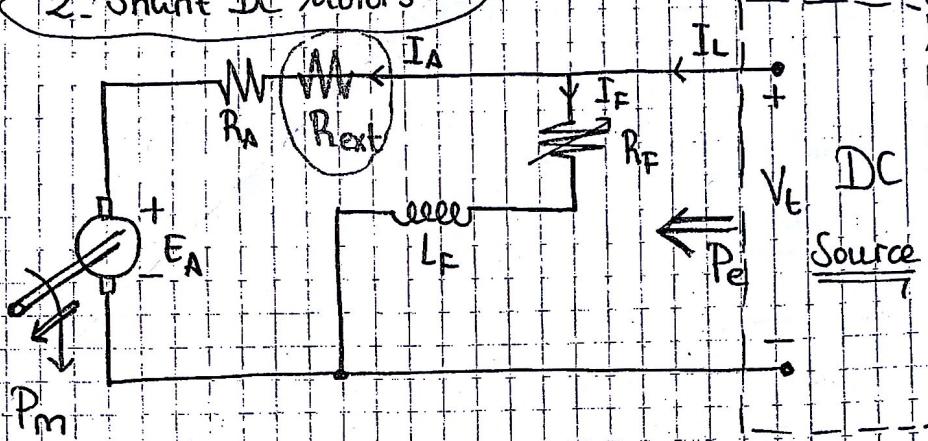

$$P_e = P_{in} = V_t I_L$$

$$P_{out} = P_m = \gamma_m w$$

Torque
(N.m)

angular velocity (rad/sec)

TORQUE-SPEED CHARACTERISTICS
OF SHUNT DC MOTOR

$$V_t = R_A I_A + E_A$$

$$\gamma = K\phi I_A$$

$$I_A = \frac{\gamma}{K\phi}$$

$$V_t = R_A \frac{\gamma}{K\phi} + K\phi w$$

$$K\phi w = V_t - R_A \frac{1}{K\phi} \gamma$$

$$w = \frac{1}{K\phi} \left(V_t - \frac{R_A}{(K\phi)^2} \gamma \right)$$

$$E_A = K\phi w$$


$$\gamma = K\phi I_A$$

magnetic field produced by field windings

The relationship between torque and speed of a shunt dc motor

$(T-w)$ characteristic depends on ϕ, R_A, V_t

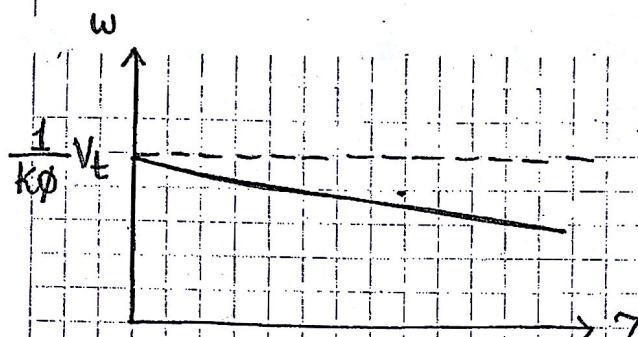
$$\phi = \frac{V_t}{R_F} \frac{I_F}{I_a}$$




hız azaldıkça
yük gönderilen güç ↑
değşim lineer

The torque speed characteristics
of a shunt dc motor

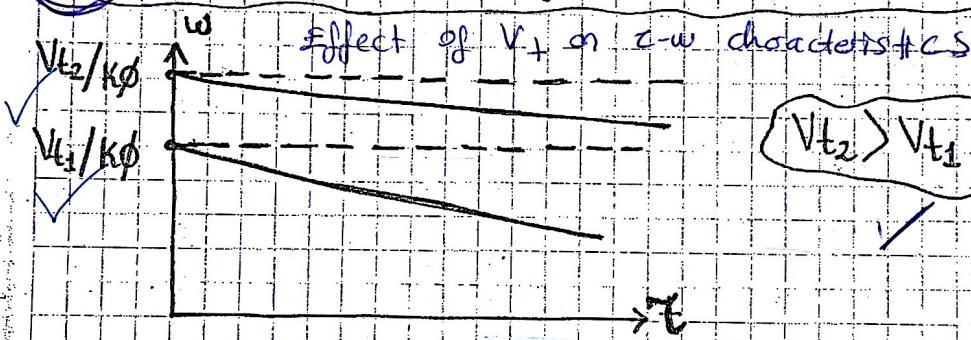i) Effect of terminal voltage on the torque-speed characteristics




$$Vt_2 > Vt_1$$

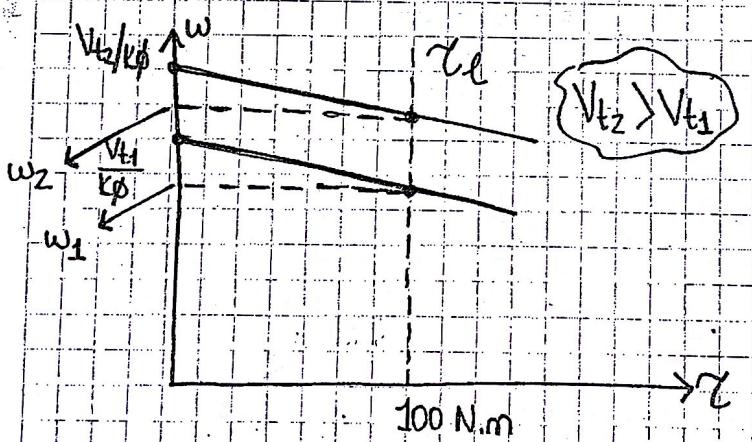

terminal volajı ↑
hız (motor için) ↑
ya da tam tersi

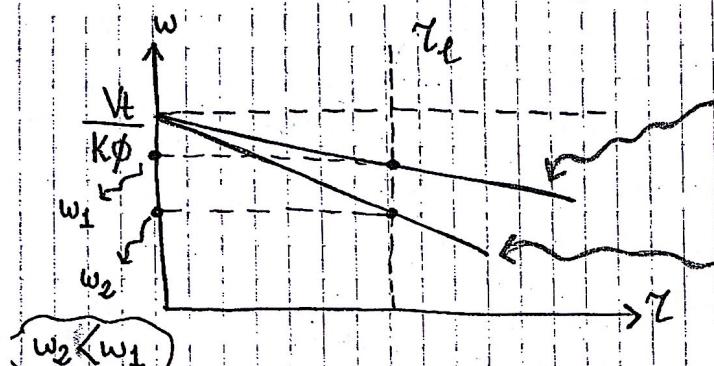ii) Effect of R_A on (γ - w) Characteristics



$$\left(-\frac{R_A}{K\phi} \right)$$

$$R_A = R_{A1}$$

egim

$$\frac{-R_A}{(K\phi)^2}$$

mi alnali

$$R_{A2} > R_{A1}$$

Referat


direct

$$R_A \uparrow \Rightarrow w \downarrow$$

R_{ext} direnci eklenildiginde
decrease

$$w = \frac{1}{K\phi} V_t - \frac{(R_A + R_{ext})}{(K\phi)^2} \gamma$$

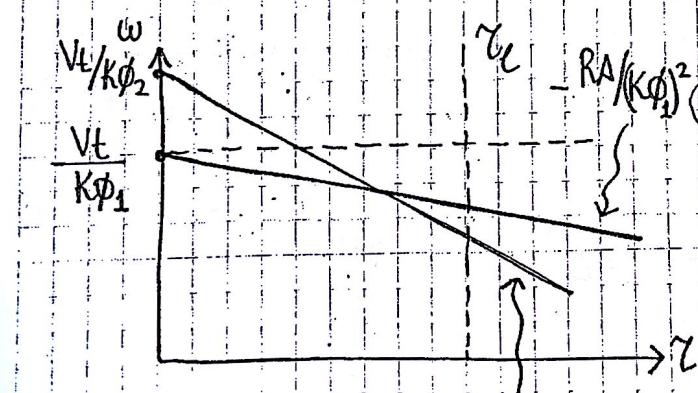iii) Effect of R_F on (γ - w) Characteristics




$$-R_A/(K\phi_1)^2$$

γ_L : load torque

is assumed to be constant

$$w = \frac{1}{K\phi} V_t - \frac{R_A}{(K\phi)^2} \gamma$$
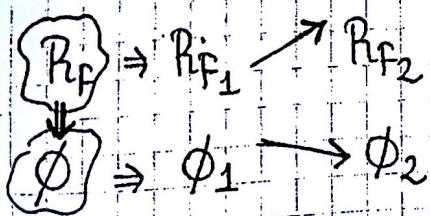
$$I_F = \frac{V_F}{R_F} = \frac{V_t}{R_F}$$



$$R_F \uparrow \Rightarrow I_F \downarrow \Rightarrow \phi \downarrow$$

* The speed of a shunt DC Motor can be adjusted by;

1) Varying terminal voltage (V_t) ✓

2) varying field circuit resistance (R_f) ✓


3) Inserting external resistance in series with motor. ✓

Kayıplar yüksek

$$P_{loss} = R_{ext} I_A^2$$

Sınav öncesi

3-Series DC Motors

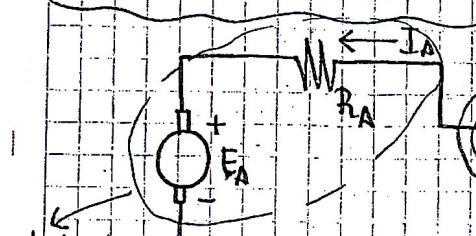

stator'un
esdeğer dairesi

rotor'un esdeğer dairesi

I_L

$$V_t = E_A + (R_s + R_A) I_A$$

Manyetik alan
oluyuyor...

DC voltaj uygulan-
digi icin L_s 'nin
üzerinde herhangi
bir voltaj düşüsü
yok, L_s hesaba
katilmam...

$$V_t = K\phi w + (R_s + R_A) \frac{\gamma}{K\phi}$$

$$\gamma = K\phi I_A = K K_1 I_A I_A \Rightarrow K K_1 I_A^2$$

$$I_A = \sqrt{\frac{\gamma}{K K_1}}$$


$\phi \propto I_A \Rightarrow K_1$: constant value

$$\phi = K_1 I_A = K_1 \sqrt{\frac{\gamma}{K K_1}} = \sqrt{\frac{K \gamma}{K_1}}$$

$$V_t = K \sqrt{\frac{K_1 \gamma}{K}} w + (R_s + R_A) \sqrt{\frac{\gamma}{K K_1}}$$

$$V_t = \sqrt{K K_1 \gamma} w + (R_s + R_A) \sqrt{\frac{\gamma}{K K_1}}$$
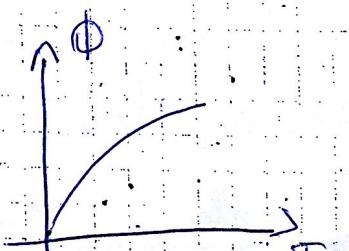
$$\sqrt{K K_1 \gamma} w = V_t - (R_s + R_A) \sqrt{\frac{\gamma}{K K_1}}$$




$$\phi = K_1 I_S$$

Linear Reg. on

haftaya → Çarşamba 2. saat Quiz

34-a
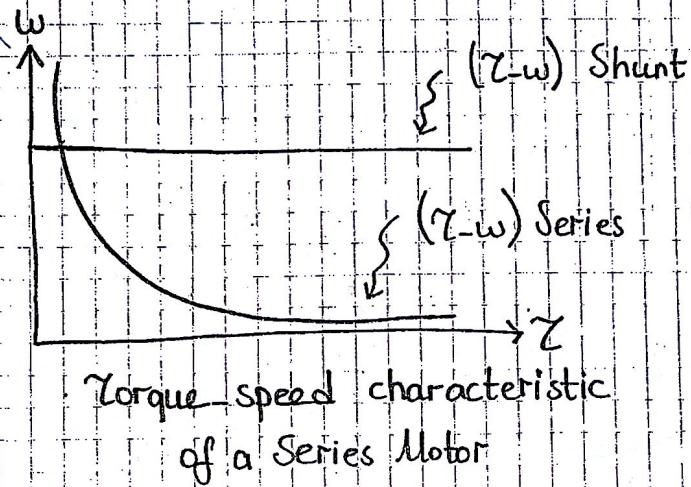
$$\omega = \frac{1}{\sqrt{KK_1}} V_t - \frac{(R_s + R_A)}{KK_1} \rightarrow \underline{\underline{\zeta = 0 \quad \omega = \infty}}$$



Torque speed characteristic
of a Series Motor

Sabit hız istersek
tercihimiz Shunt olsalıdır
çünkü hız, yükteki değişimlerde
etkilenmiyor.

Öncek, series de yükteki
herhangi bir artış
hızı etkiliyor, ve değişim
oldukça fazla oluyor.


Seri DC Motor \rightarrow "yoksuz" durumda, basta çalıştırılmaz!

* * Series DC Motor is not used for no load operations
At no-load condition the speed of motor is very high.


$\underline{\underline{\zeta = 0, \omega \nearrow \infty}}$
(ζ : load ω : speed)

4- Permanent Magnet Motors (PMM)

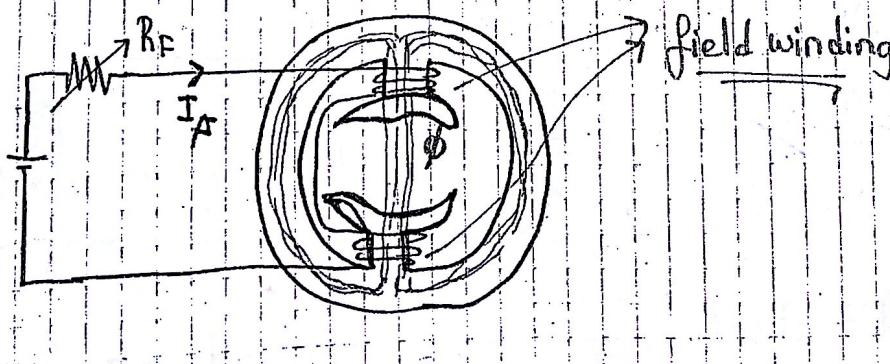
In this type motors there is no field winding. The magnetic field is produced using magnetic materials...



COMPOUNDED MOTOR - (SERİ + PARALEL)

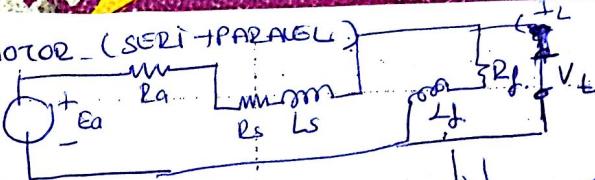

35

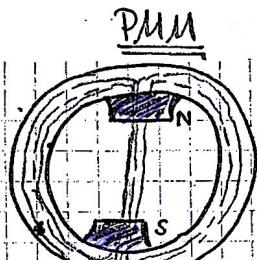

Maliyeti
düşük

No field winding

dünyada güçte olan shunt motor ile PMM
karsılıstırılsınsa;

- ✓ • PMM' nin Volumu küçük
- ✓ • Allan sorgusu yok $\Rightarrow P_{loss} = R_f I_f^2$ yok
- ✓ • PMM yüksek güçlerde kullanılmaz
(guc $\leq 1\text{KW}$)

Shunt Motor

- Volume büyük
- P_{loss} var
- "yüksek" güçlerde kullanılır.

Field
winding
var

PMM

- Volume küçük \Rightarrow (aynı güçte)
- P_{loss} yok
- "yüksek" güçlerde kullanılır.

Field
winding
yok

$$1 \text{ hP} = 746 \text{ W}$$

Example:

A 50-hp, 250-V, 1200 r/min dc shunt motor has an armature ~~resistance~~ resistance of $0,06\Omega$. It is field current has a total resistance of 50Ω , which produces a no-load speed of 1200 r/min. There are 1200 turns per pole on the shunt field winding.

a) Find the speed of this motor when its input current is 100A


b)

c)

200A

300A

35-a

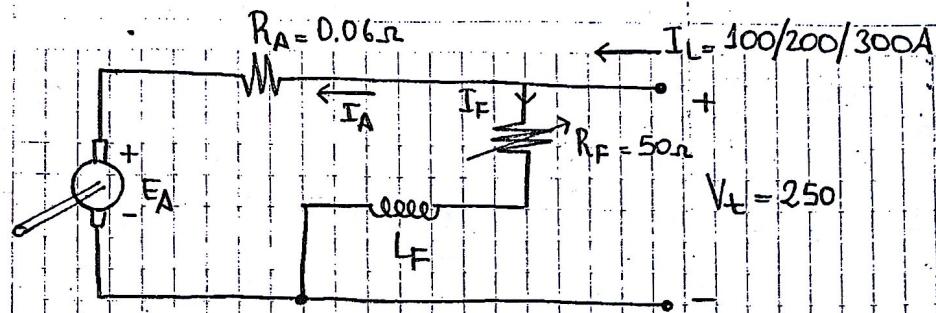

{ At no-load $n_r = 1200 \text{ rpm (r/min)}$

$$\Rightarrow \gamma = 0 \Rightarrow \gamma = K\phi I_A = 0$$

$$I_A = 0$$

$$V_t = R_A I_A + E_A = 0 + E_A \Rightarrow E_A = 250V$$

$$\left\{ \begin{array}{l} E_A = 250V \\ n_r = 1200 \text{ rpm} \end{array} \right.$$

a) $I_F = \frac{250}{50} = 5A$ ✓

$$I_A = I_L - I_F = 100 - 5 = 95$$

$$E_A = V_t - R_A I_A = 250 - 0.06 \times 95 = 244.3V$$

$$\frac{E_{A1}}{E_{A2}} = \frac{K\phi_1 w_1}{K\phi_2 w_2} = \frac{\phi_1 n_1}{\phi_2 n_2} = \frac{1200}{n_2} = \frac{250}{244.3} \Rightarrow n_2 = 1173 \text{ rpm}$$

b) $I_L = 200A$

$$I_A = 200 - 5 = 195$$

$$E_A = 250 - 0.06 \times 195 = 238.3V$$

$$\frac{E_{A1}}{E_{A2}} = \frac{K\phi_1 w_1}{K\phi_2 w_2} = \frac{1200}{n_2} = \frac{250}{238.3}$$

$$\Rightarrow n_2 = 1144 \text{ rpm}$$

$$c) I_L = 300A \Rightarrow I_A = 300 - 5 = 295A$$

$$E_A = 250 - 0.06 \times 295 = 232.3V$$

$$\frac{1200}{n_2} = \frac{250}{232.3} \Rightarrow n_2 = 1175 \text{ rpm}$$


| | |
|---------------------|--------|
| $I_A = 0$ (no load) | 1200 ✓ |
| $I_A = 100$ | 1173 ✓ |
| $I_A = 200$ | 1144 ✓ |
| $I_A = 300$ | 1115 ✓ |

n (rpm)

6 Nisan Garsamba 2011

Starters in DC Motors.

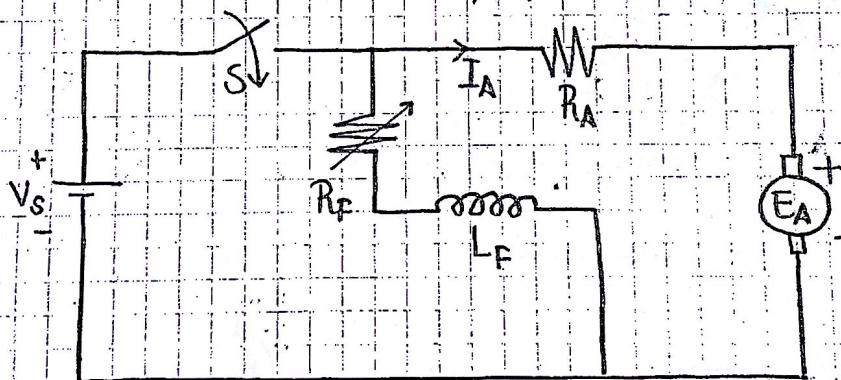The starting current of DC motors is very high and should be limited to obtain a proper operation.



Switch S is closed at $t=0$

$$V_s = R_A I_A + E_A \Rightarrow I_A = \frac{V_s - E_A}{R_A}$$

$$E = K\phi w \Rightarrow I_A = \frac{V_s - K\phi w}{R_A}$$

At starting $n=0$ or $w=0 \Rightarrow E_A(t=0^+) = 0$

* $I_A = \frac{V_s}{R_A} \Rightarrow I_A(\text{starting})$

Example: for a shunt DC Motor with armature resistance of 0.02Ω
find the starting current.


The motor is supply from a 200Vdc source

$$\left. \begin{array}{l} V_s = 200 \\ R_A = 0.02 \end{array} \right\} I_A(\text{starting}) = \frac{200}{0.02} = 10000A$$

Stators \Rightarrow DC motorlarda motorun başlangıç akımı çok yüksek olduğu için, bu durumun "ön"ine girmeye yarayan cihazlardır... akım

ex: DC motorun nominal değeri $\Rightarrow 50A$ iken
starting akım değeri $\Rightarrow 1000A$

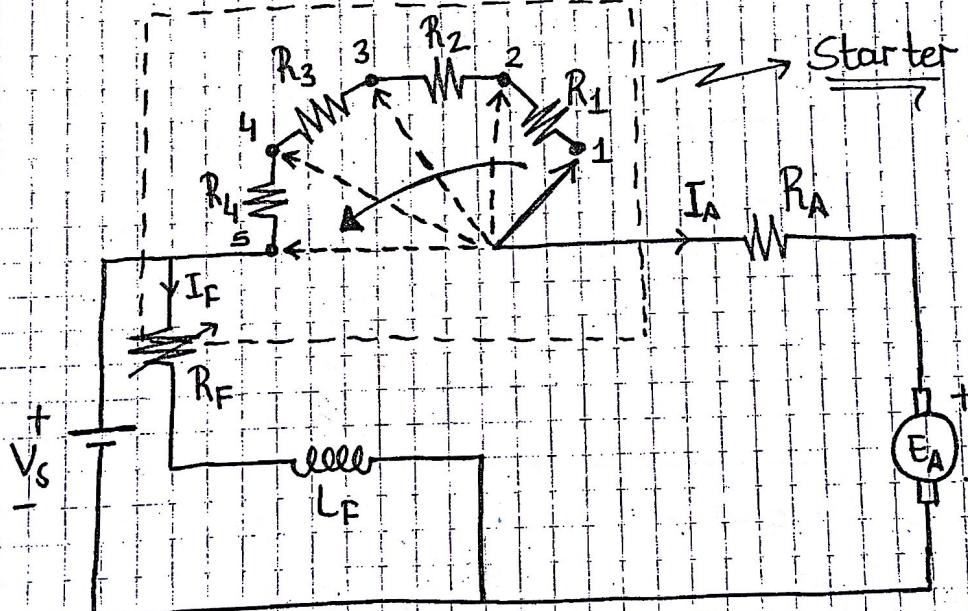Starting akım değerini düşürmeye yarayan \Rightarrow starters




$$At t=0 \rightarrow I_A = \frac{V_s - K\phi w}{R_A + [R_1 + R_2 + R_3 + R_4]}$$

$$w(t=0)=0 \rightarrow I_A(t=0) = \frac{V_s}{R_A + R_1 + R_2 + R_3 + R_4}$$


$$\omega \uparrow \Rightarrow E_A \uparrow \Rightarrow I_A \downarrow$$

with increasing of motor speed the armature current decreases

$$I_A = \frac{V_s - K\phi w}{(---)}$$

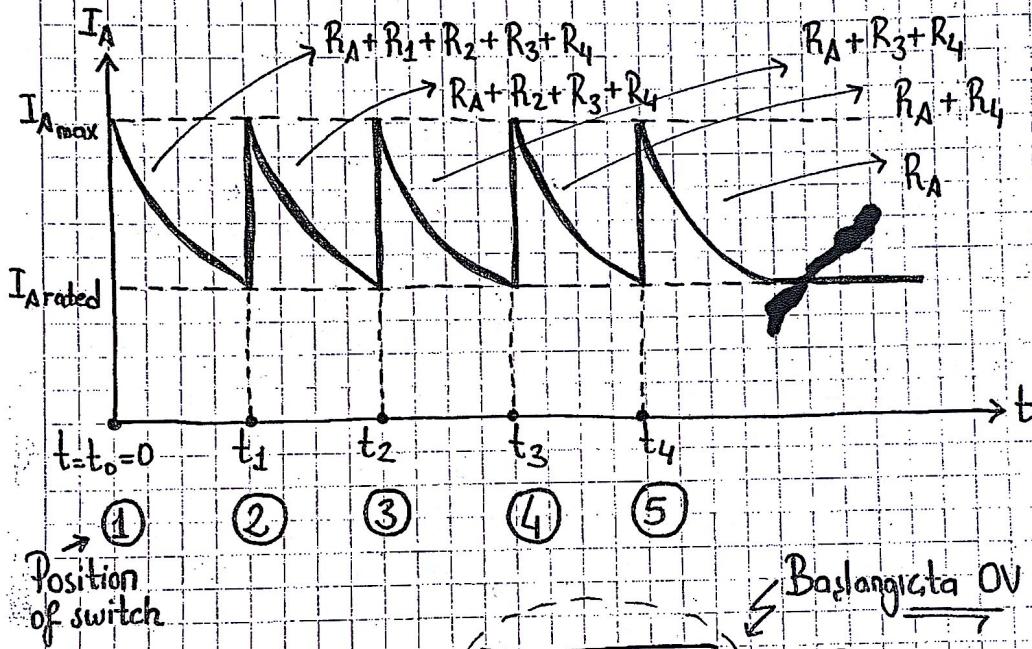


Position
of switch

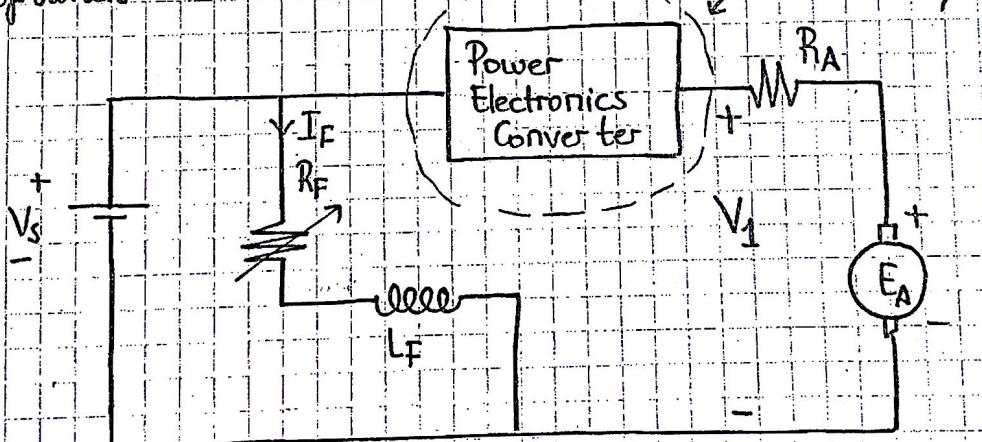

V_1 (voltage applied to motor) is adjusted using a converter.
 V_1 is increased from zero up to voltage rating of motor.

Faraday's Law

37-a.

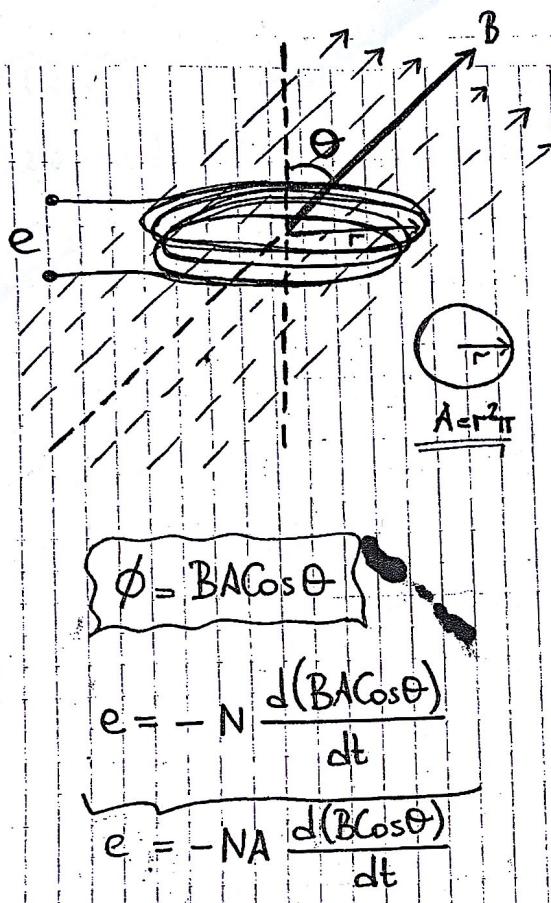

$$e = -N \frac{d\phi}{dt}$$

N: turns number of coil
 ϕ : magnetic flux (Weber)

$$B = \frac{\phi}{A}$$

Magnetic flux density (Tesla)


$$\theta = 0^\circ \Rightarrow \phi_{\max}$$

$$\theta = 90^\circ \Rightarrow \phi_{\min}$$

7 Nisan Persembe 201

Quiz
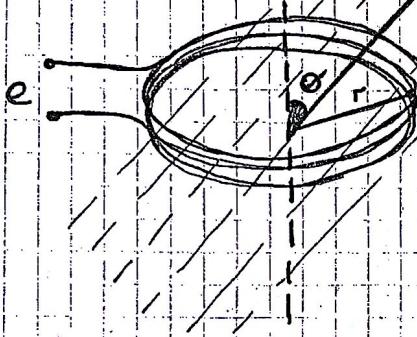
$$\text{#1} \Rightarrow B = 2 \sin \omega t, \omega = 2\pi f, f = 50 \text{ Hz}, N = 100$$



$$e = -N \frac{d\phi}{dt}$$

$$\Rightarrow -100 A \cos \theta \frac{12 \sin \omega t}{dt}$$

$$\Rightarrow e = -200 A \cos \theta \omega \cos \omega t$$

$$e = -200 A 2\pi f \cos \theta \cos \omega t$$

$$\phi = BA \cos \theta$$

$$e = -100 \frac{dBA \cos \theta}{dt} = -100 A \cos \theta \frac{dB}{dt} = -100 A \cos \theta \frac{di}{dt}$$



$$e = -20000 \pi A \cos \theta \cos \omega t$$

$$\text{#2} \Rightarrow B = 2 \text{ Tesla} \text{ coil is stationary find } e = ?$$

$$A = r^2 \pi$$

$$\phi = AB \cos \theta$$

$$e = -100 \frac{d\phi}{dt}$$

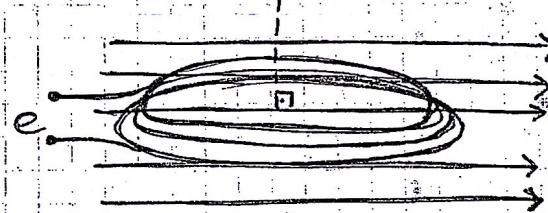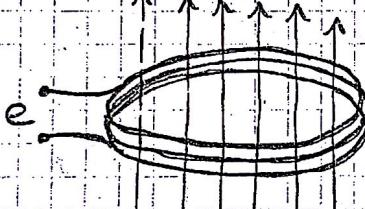

$$\phi_{\max}$$

$$\theta = 0^\circ$$

$$\theta = 90^\circ$$

$$\phi_{\min} = 0$$

$$e = -N \frac{dBA \cos \theta}{dt}$$

$$\rightarrow -NBA \frac{d \cos \theta}{dt} = 0$$

$(B, A, \theta \Rightarrow \text{constant variable})$

$$\text{#3} \Rightarrow B = 2 \text{ Tesla}, \text{ the coil rotates with } 3000 \text{ rpm}$$

$$\theta = \omega t$$

$$\rightarrow \theta = \frac{3000 \times 2\pi t}{60} = \frac{100\pi t}{60}$$

$$e = -100 \frac{dBA \cos \theta}{dt} = -100 A B (100\pi t) \sin \theta$$

$(B, A \Rightarrow \text{constant})$

$$(e = 20000 \pi A \sin 100\pi t)$$

#4) $\Rightarrow B = 2 \text{ Tesla}$, The magnetic field rotates clockwise with speed of 3000 rpm and the coil rotates counterclockwise with the same speed, find e ?

$$\theta = wt \rightarrow \theta = \frac{3000}{60} \times 2\pi t + \left[\frac{3000}{60} \times 2\pi t \right]$$

$$\theta = 200\pi t$$

$$e = -N \frac{dBA \cos \theta}{dt} = 100(2)(1)(200\pi) [\sin 200\pi t]$$

$$e = 40000\pi A (\sin 200\pi t)$$

#5) $\Rightarrow B = 2 \text{ Tesla}$, the magnetic field and the coil rotates at the same direction with speed of 2000 rpm

$$e = -N \frac{d\theta}{dt} = -N \frac{dBA \cos \theta}{dt} = NBA \frac{d \cos \theta}{dt} = 0$$

$B, A, \theta \Rightarrow$ Constant Variable...

#6) $\Rightarrow B = 2 \sin wt$, coil and field rotates at the same direction with speed of 4000 rpm.

$$e = -N \frac{d\theta}{dt} = -N \frac{dBA \cos \theta}{dt} = -NA \cos \theta \frac{dB}{dt}$$

$$e = -NA \cos \theta \left(\frac{d2 \sin wt}{dt} \right)$$

$$e = -NA \cos \theta [2w \cos wt]$$

#7 $\Rightarrow B = 2 \sin \omega t$, the magnetic field rotates with speed of n_1 (clockwise) and the coil rotates with speed of n_2 (counter-clockwise), find e ?

$$e = -N \frac{d\phi}{dt} \Rightarrow e = -N \frac{dB A \cos \theta}{dt} = -NA \frac{dB \cos \theta}{dt}$$

$$e = -NA \left[(\cos \theta) \frac{dB}{dt} + B \frac{d \cos \theta}{dt} \right]$$

$$\theta = \left[\frac{n_1}{60} \times 2\pi t \right] + \left[\frac{n_2}{60} \times 2\pi t \right]$$

$$\theta = \frac{(n_1 + n_2)}{60} \times 2\pi t$$

$$e = -NA \left\{ \left(\cos \frac{n_1 + n_2}{60} 2\pi t \right) [2w \cos \omega t] + (2 \sin \omega t) \left(\frac{n_1 + n_2}{60} 2\pi \right) \sin \frac{n_1 + n_2}{60} \right\}$$

$$e = -NA \left\{ \left[\cos \left(\frac{n_1 + n_2}{60} 2\pi t \right) \right] [2w \cos \omega t] + \left[2 \sin \omega t \right] \left[\frac{n_1 + n_2}{60} 2\pi \right] \sin \frac{n_1 + n_2}{60} \right\}$$

4/5
Soru
Vize igin


2 - DC Machine (1 yada 2 soru)
3 - Tanim
4 - Trafo

39-a

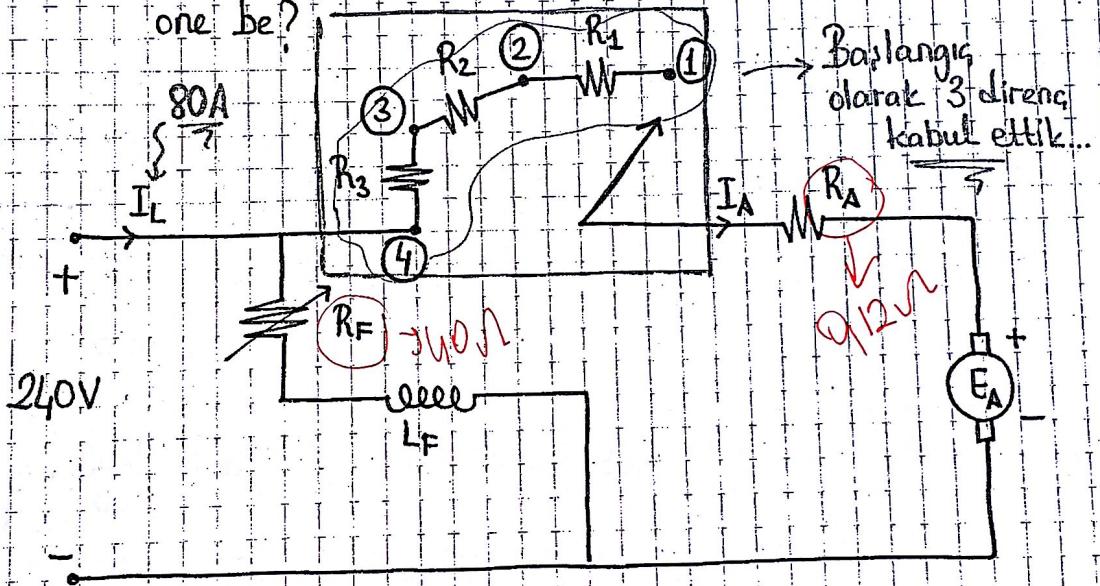Example

An automatic starter circuit is to be designed for a shunt motor at 20hp, 240V and 80A.

The armature resistance of the motor is 0.12Ω and the shunt field resistance is 40Ω. The motor is to start with no more than 250 percent of its rated armature current, and as soon as the current falls to rated value, a starting resistor stage is to be cut out. How many stages of starting resistance are needed and how big should each one be?




$$R_A = 0.12\Omega$$

$$R_F = 40\Omega$$


$$V_T = E_A + I_A R_A$$

$$V_T = K\phi w + I_A R_A$$

$$I_A = \frac{V_T - K\phi w}{R_A}$$

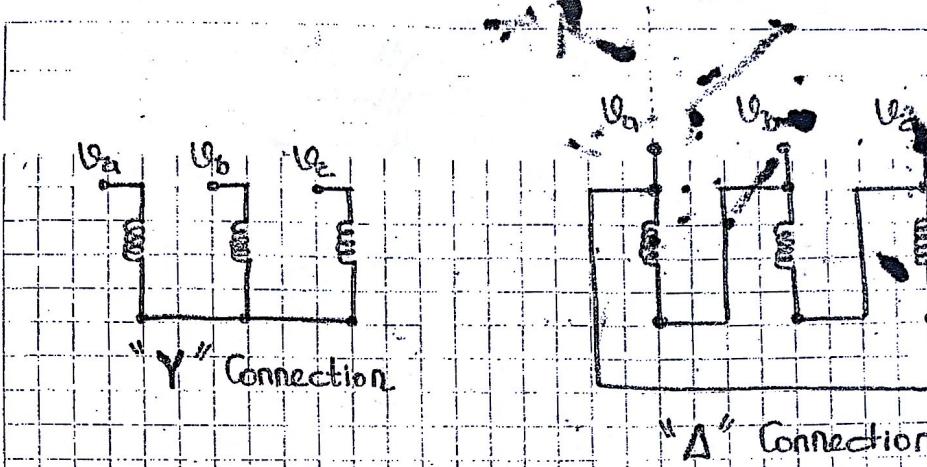

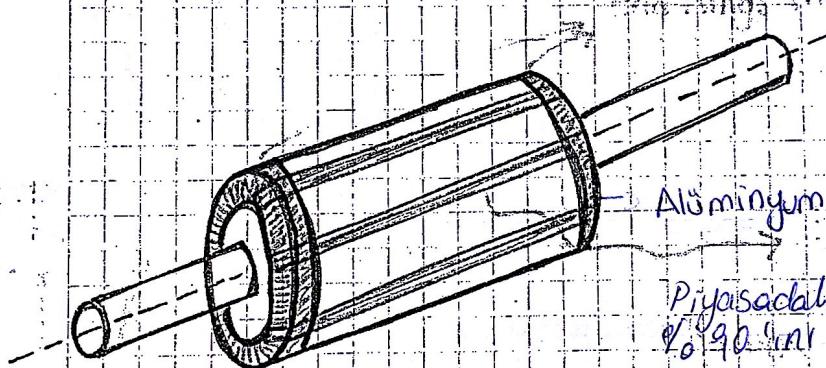Rotor { a - Squirrel - Cage type
b - Wound - Rotor type



Alüminyum yada bakır ile doldurulur
(bir kafes gibi)

Piyasadaki eniclesyon motorlarının
% 90'ını boyaledir.

Squirrel - Cage type Rotor → tel kullanılmaz, dokum
(Sincap Kafes) olarak üretilir

* The squirrel-cage rotor consists of conducting bars placed in the slots and short circuited at both ends.

* The wound rotor consists of a distributed windings, similar to that of stator.

The terminals of windings are brought out to slip-rings for external connection.

- 3 magnetic fields are produced inside the machine
- $(H_{A+}) + (H_{B-}) + (H_{C-})$ A rotating field magnetic fields is produced by a rotating field magnetic fields.
- These 3 magnetic fields are produced by these 3 magnetic fields.
- The speed of this magnetic field (rotating field) is constant and is equal to magnetic field (field).

msu

$$f = \frac{d}{dx} f(x)$$

• magnetic field, (spherical spreads) f: frequency of applied voltage at outlet
• numbers of people (even numbers)

The rotating magnetic field rotates with a constant speed in the induction machine

$$F(\theta, t) = \frac{3}{2} \max_{\omega} C_0 s(\omega t - \theta)$$


$$\cos(\theta + \omega t) + \cos(\omega t + \theta - 240^\circ) + \cos(\omega t + \theta - 120^\circ) = 0$$

$$= \cos(\theta + \omega t) + \cos(\omega t + \theta - 240^\circ) + \cos(\omega t + \theta - 480^\circ)$$

Operational Principles

* When the stator is excited with 3-phase balanced ac currents, a rotating mmf (F_s) is created in the air-gap.

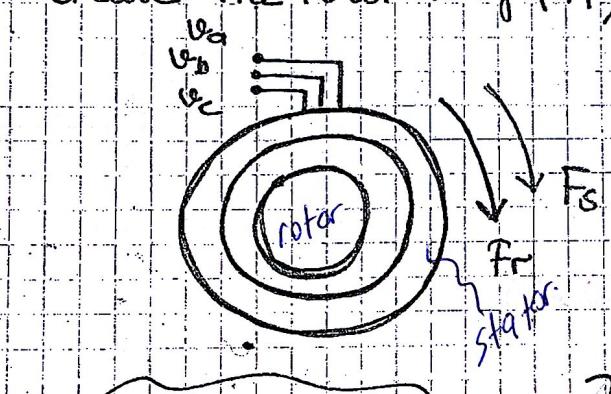* The rotating mmf (F_s) generated by stator will induce voltages and currents in the rotor windings which will create the rotor mmf (F_r)



r_1 : resistance of stator windings

x_1 : leakage reactance of stator windings

r_2 : rotor resistance

x_2 : leakage reactance of rotor

n_s : speed of rotating magnet field

n_r : the speed of rotor

Slip


$$s = \frac{n_s - n_r}{n_s}$$

$$n_r = (1-s)n_s$$

haftaya Perseble
Over
28 Nisan

$$r'_2 + \left(\frac{n_s}{n_r}\right)^2 r_2$$
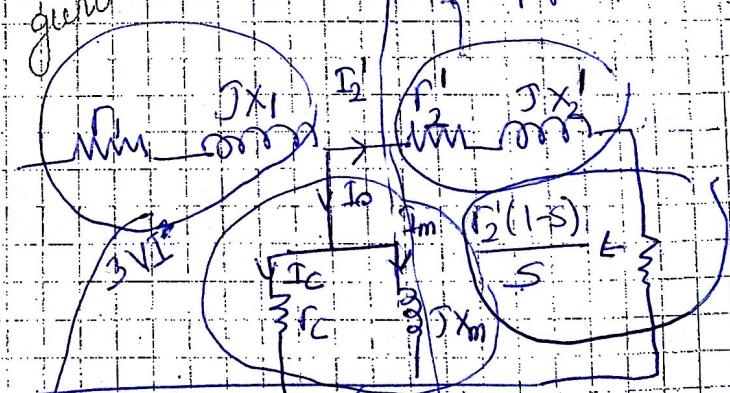
$$x'_2 = \left(\frac{n_s}{n_r}\right) x_2$$



stator winding
equivalent
circuit

equivalent circuit
of cor.

Pq
954

starting P=3Vc Icosθ


44-a

Midterm

Question #1:

✓ Permeability $\mu = \infty \Rightarrow$ nıve direnci ($R=0$)

Sadece gap ditencileri hesapla...

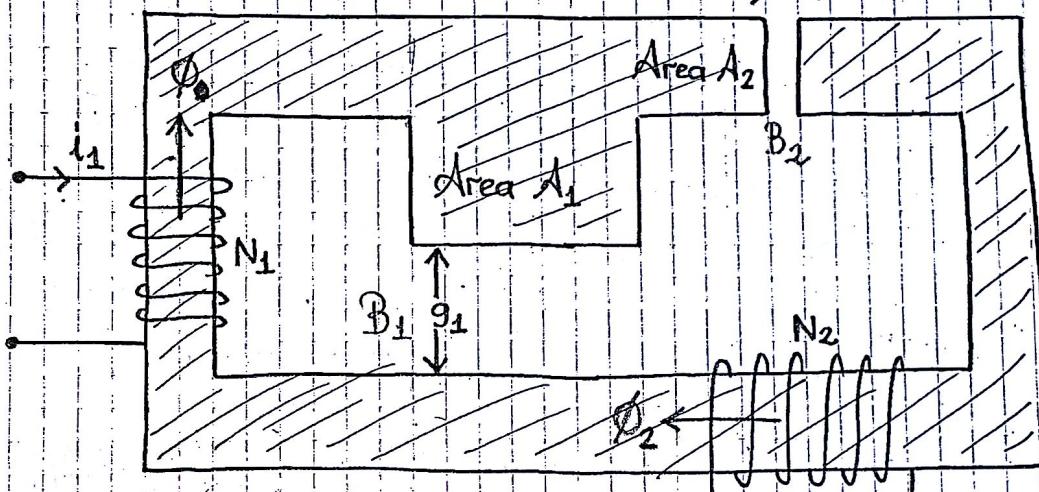

$(\mu_r = \infty \Rightarrow M_r \text{ degeri çok büyük}) \uparrow i_2$

a) $i_1 = I_1, i_2 = 0$

- Determine the magnetic flux of winding 1
- Determine the magnetic flux of winding 2
- Determine the magnetic flux densities of airgaps ① and ②

b) $i_1 = 0, i_2 = I_2$


Repeat the questions of part a)

c) $i_1 = I_1, i_2 = I_2$

Repeat the questions of part a)

$$\mu_0 = 4\pi \times 10^{-7}$$

45

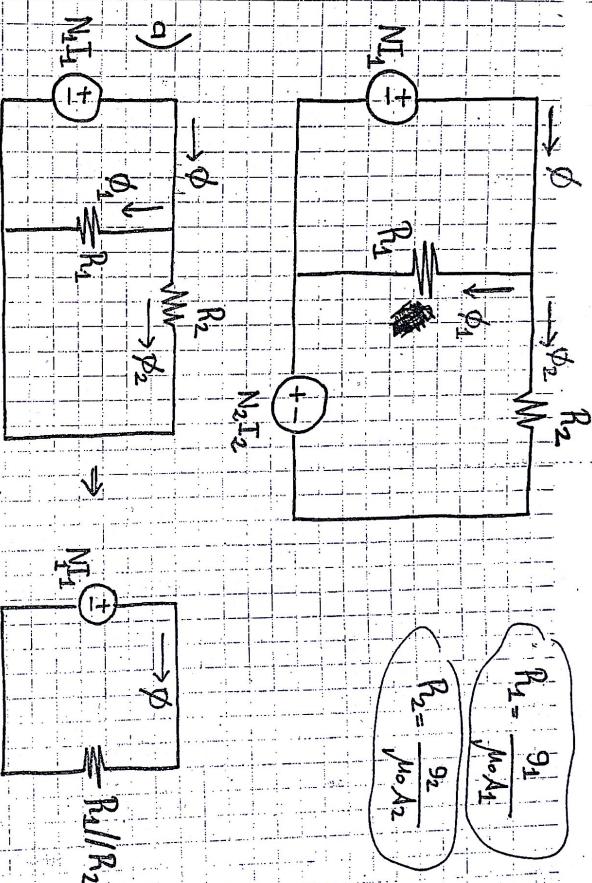

$$a) \quad \frac{R_1 // R_2}{R_1 + R_2} \rightarrow \phi$$

$$N_1 I_1 = \phi \left(\frac{R_1 // R_2}{R_1 + R_2} \right) = \phi \frac{R_1 R_2}{R_1 + R_2}$$

$$N_2 I_2 = \phi \left(\frac{R_2}{R_1 + R_2} \right) = \phi \frac{R_2}{R_1 + R_2}$$

$$R_1 = \frac{\phi_1}{\mu_0 A_1}$$

$$R_2 = \frac{\phi_2}{\mu_0 A_2}$$

$$\left(R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$N_1 I_1 = \phi \left(\frac{R_1 R_2}{R_1 + R_2} \right) = \phi \frac{N_1 I_1 \left(\frac{\phi_1}{\mu_0 A_1} + \frac{\phi_2}{\mu_0 A_2} \right)}{R_1 + R_2}$$

$\phi = \frac{N_1 I_1 \left(\frac{\phi_1}{\mu_0 A_1} + \frac{\phi_2}{\mu_0 A_2} \right)}{R_1 + R_2}$


*Sorgfältig nachrechnen
gegen ok!*

$$\phi = \frac{N_1 I_1}{R_1 R_2} = \frac{N_1 I_1 (R_1 + R_2)}{R_1 R_2}$$



$$\phi = \frac{N_1 I_1}{R_1 R_2} \quad \phi_1 = \frac{N_1 I_1}{R_1}$$

$$\phi = \phi_1 + \phi_2$$

a)

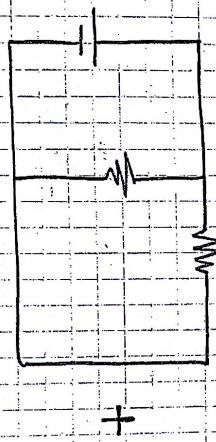

b)

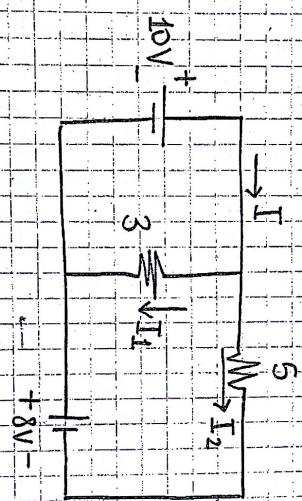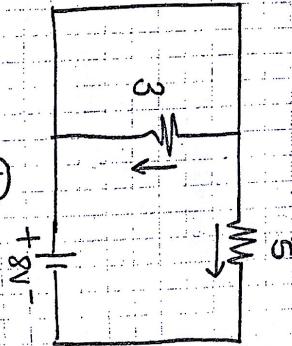

Devore Teorico

$$\begin{aligned}\phi_c &= \phi_a + \phi_b \\ \Phi_{dc} &= \Phi_{2a} + \Phi_{2b} \\ B_{dc} &= B_{2a} + B_{2b}\end{aligned}$$

c)

$$\begin{aligned}\phi_c &=? \\ B_1, B_2 &=?\end{aligned}$$

C)

$$\phi = \phi_a + \phi_b$$




46


* Induction Machines:

$$n_s = \frac{120f}{P} \text{ (rps)}$$
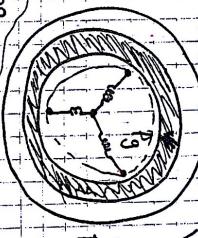
$$\ast n_s = \frac{2f}{P} \text{ (rps)}$$



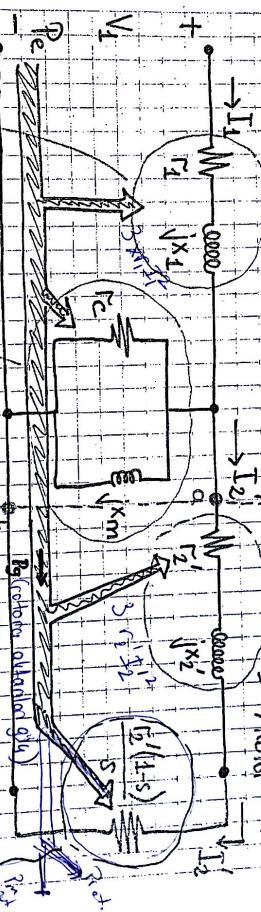Equivalent Circuit of an Induction Machine (IM) Eq. Circuit of



Per phase
Equivalent Circuit of an IM#
Circuit of Stator Winding
Core $\frac{3}{2} \frac{C}{C}$

Equivalent Circuit of an IM#

$$P_e = 3V_1 I_1 \cos \phi$$

$$P_{intm} = \frac{I_2'^2 (1-s)}{s} * \frac{1}{2} I_2'^2$$

\hookrightarrow internal mechanical power

for a 3-Phase IM

$$P_{int-m} = 3 \times \frac{r_2' (1-s)}{s} I_2'^2 \quad * \times \times$$

Torque - Speed Characteristic of an IM

$$\begin{aligned} P_m &= \gamma w_r \\ \text{Power} & \quad \text{Angular Velocity of rotor} \\ (\text{W}) & \quad (\text{rad/sec}) \\ (\text{mechanisch} \quad \text{Torque} \\ \text{gesch.)}) & \quad (\text{Nm}) \end{aligned}$$

$$3 \times \frac{r_2' (1-s)}{s} I_2'^2 = P = \gamma w_r$$

$$\gamma = \frac{3r_2' (1-s)}{sw_r} I_2'^2$$

$$s = \frac{n_s - n_r}{n_s} = \frac{w_s - w_r}{w_s}$$

$$\begin{aligned} n_r &= (1-s)n_s \\ w_r &= (1-s)w_s \end{aligned}$$

$$w_r = (1-s)w_s \quad \checkmark$$


$$\Rightarrow \gamma = \frac{3 \times r_2' (1-s)}{s(1-s)w_s} * I_2'^2 = \frac{3r_2' I_2'^2}{sw_s}$$

$$\gamma = \frac{3r_2' I_2'^2}{sw_s}$$

47-a

MOTOR UN PERFORMANCE ANALYSIS

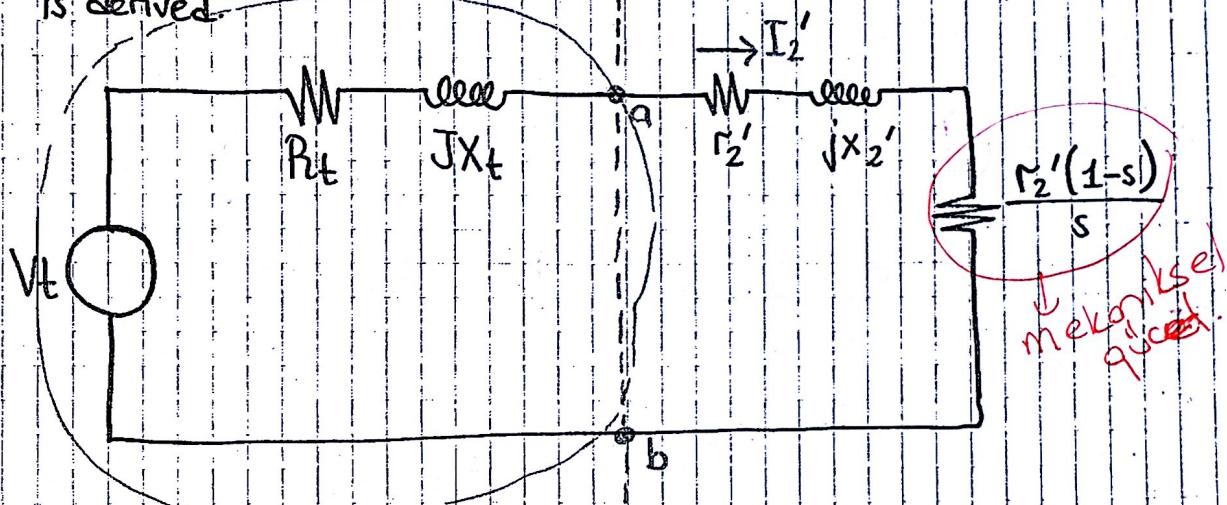→ Using the Thevenin's Law the equivalent circuit between a and b is derived.



$$V_t = \frac{|(R_c // jX_m)|}{|((r_c // jX_m) + r_1 + jX_1)|} * V_1$$


$$R_t + jX_t = (r_1 + jX_1) // r_c // jX_m$$

$$I_2' = \frac{V_t}{\sqrt{(R_t + \frac{r_2'}{s})^2 + (X_t + X_2')^2}}$$

$$P = C \cdot \omega_r^{\text{rad/s}}$$

$$\gamma = \frac{3r_2'}{sWS} * \frac{V_t^2}{(R_t + \frac{r_2'}{s})^2 + (X_t + X_2')^2}$$

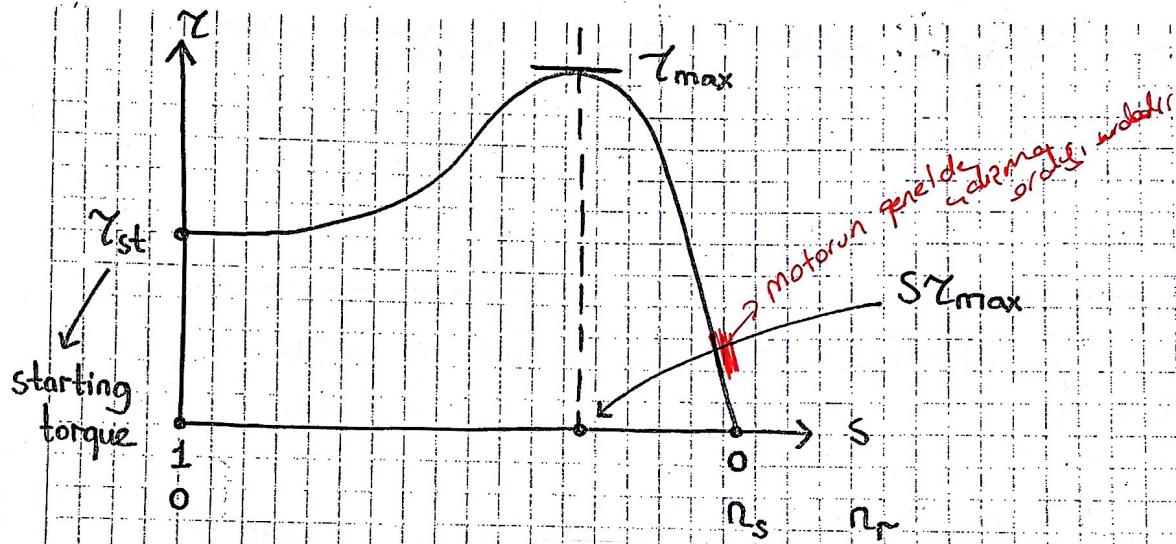ASENKRON MOTOREN: MOMENT - HIZ KARAKTERISTIGI



T - n characteristic of an IM

| S | n_r | n_s |
|-----|----------|----------|
| 0 | n_{r1} | n_{s1} |
| 0.1 | n_{r2} | n_{s2} |
| 0.2 | n_{r3} | n_{s3} |
| 1 | n_r | n_s |
| 1 | | |

$$T(n=n_s) = 0$$

motorsenkron hızda
kuvvet düşer.
Buna asenkron motor
(induction motor)
denir.

50-a

$$P_g = \gamma w_s$$

w_r or w_m → rotor → $\frac{\pi r}{60} 2\pi$ (rpm) (5)

w_s → sentron hız → $\frac{n_s}{60} 2\pi$ (rpm)


$$\text{Senkron hız (sabit)} \left(\frac{120f}{P} = n_s \right)$$

sebece frekansına bağlı (sbt)

dakka

$\Rightarrow \gamma$ is maximum if $(P_g = \max)$

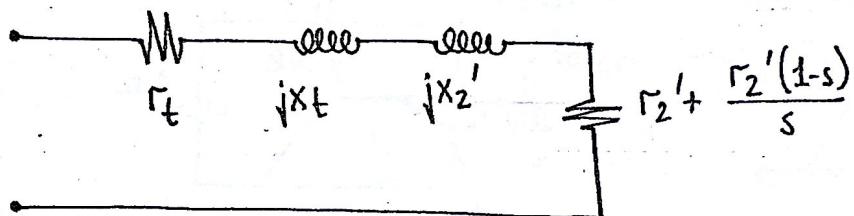
$$r_t' + \frac{r_2'(1-s)}{s} = \sqrt{r_t^2 + (x_t + x_2')^2}$$



$$\frac{r_2'}{s} = \sqrt{\dots}$$

$$S = \frac{r_2'}{\sqrt{r_t^2 + (x_t + x_2')^2}} = S\gamma_{\max}$$

max to que
*)

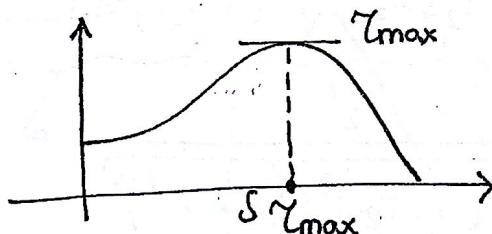

$$\text{II. y' = 0} \rightarrow \gamma = \frac{1}{w_s} * \frac{3\sqrt{t^2}}{(r_t + \frac{r_2'}{s})^2 + (x_t + x_2')^2} * \frac{r_2'}{s}$$

$y = f(x)$

$$\left(\frac{d\gamma}{ds} = 0 \right) \rightarrow S\gamma_{\max} \Rightarrow \gamma_{\max}$$

51

3-phase AC system

line to line


(51)

28 Nisan 2011

Example: A-208 volt, 10HP, 60Hz 4-pole Y-connected induction motor has a full load slip of 5% $\rightarrow s = 5\%$

- ✓ a) what is the synchronous speed of this motor?
- ✓ b) what is the rotor speed of this motor at the rated load?
- ✓ c) what is the rotor frequency of this motor at the rated load?
- ✓ d) what is the shaft torque of this motor at the rated load?

3-Phase

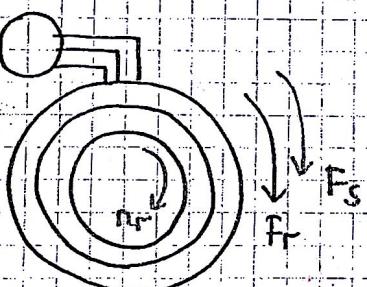
 $F_s \rightarrow$ Rotating magnetic field (stator)

 $F_r \rightarrow$ Rotating magnetic field (rotor)

n_s = synchronous speed (the speed of rotating magnetic field)

$$n_s = \frac{120f}{P}$$

f : frequency of 3-phase ac system

P : # of poles

a) $n_s = \frac{120 \times 60}{4} = \frac{1800}{4} \text{ rpm}$

$$\begin{aligned} n_s &= 1800 \\ n &= 1710 \end{aligned}$$

b) n_r = rotor speed = ?


$$s = \frac{n_s - n_r}{n_s}$$

$$\Rightarrow \frac{s}{100} = \frac{1800 - n_r}{1800}$$

$$n_r = (1 - 0.05) \times 1800 = 1710 \text{ rpm}$$

(51-a)

stator frekansı sebekeye bağlıdu.

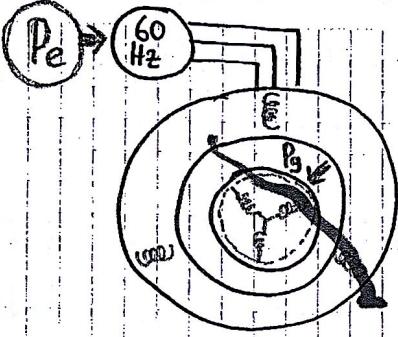

c) f_r : frequency of current or voltage of rotor windings

$$f_r = s f_s$$

$$f_r = (0.05) \times (60 \text{ Hz}) = \underline{\underline{3 \text{ Hz}}}$$

d) $\gamma_{\text{rated}} = ?$

$$P = \gamma w_r$$

$$P = 10 \times 746 = 7460 \text{ Watt}$$

$$7460 = \gamma \times \frac{1710}{60} \times 2\pi$$

$$\gamma = 41,7 \text{ (N.m)}$$

$$1 \text{ hp} = 746 \text{ Watt} \Rightarrow \cancel{x}$$

$P_{\text{out}, \text{net}}$ #
(çikış gücü)

motor dan alınabilecek
faydalı gücü

Example

A 400-V, 60Hz, 50 HP 3-phase induction motor is drawing 60 A at 0.85 PF lagging.

The stator copper losses are 2KW, and the rotor copper losses are 700W.

The friction and windage losses are 600W, the core losses are 1800W and the stray losses are neglected. Find;

a) the air-gap power, $P_g = ?$


b) the power converted?

c) power converted.

d) the efficiency

of the motor?

(52)

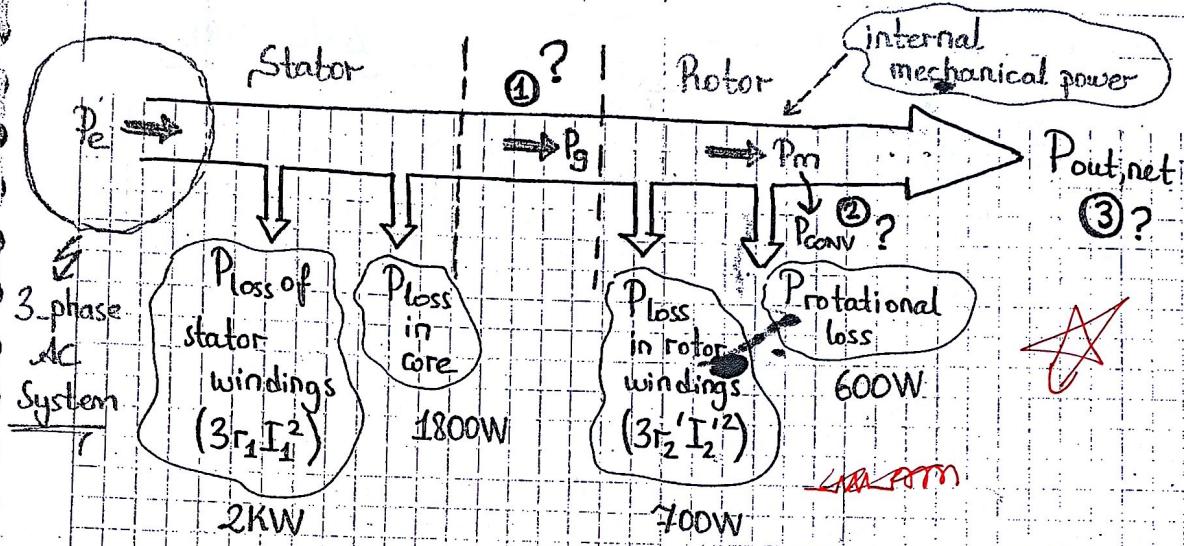

Solution:

$$P_e = \sqrt{3} V_{LL} I_e \cos \phi$$

$$P_e = \sqrt{3} (480)(60)(0.85)$$

$$P_e \Rightarrow P_e = 42400 \text{ W} \rightarrow \text{motorun elektrik sebkesinden cektili guc} = P_e$$

a) $P_g = P_e - 2K - 1800$

$$P_g = 42400 - \frac{2000}{2 \text{ KW}} - 1800 = 38600 \text{ W}$$


b) $P_{conv} = P_m$

$$P_m = P_g - 700 \cancel{\text{Watt}} \Rightarrow P_{conv} = 38600 - 700 \cancel{\text{Watt}}$$

$$P_{conv} = 37900 \text{ W}$$


c) $P_{out,net} = 37900 - 600 = 37300 \text{ W}$

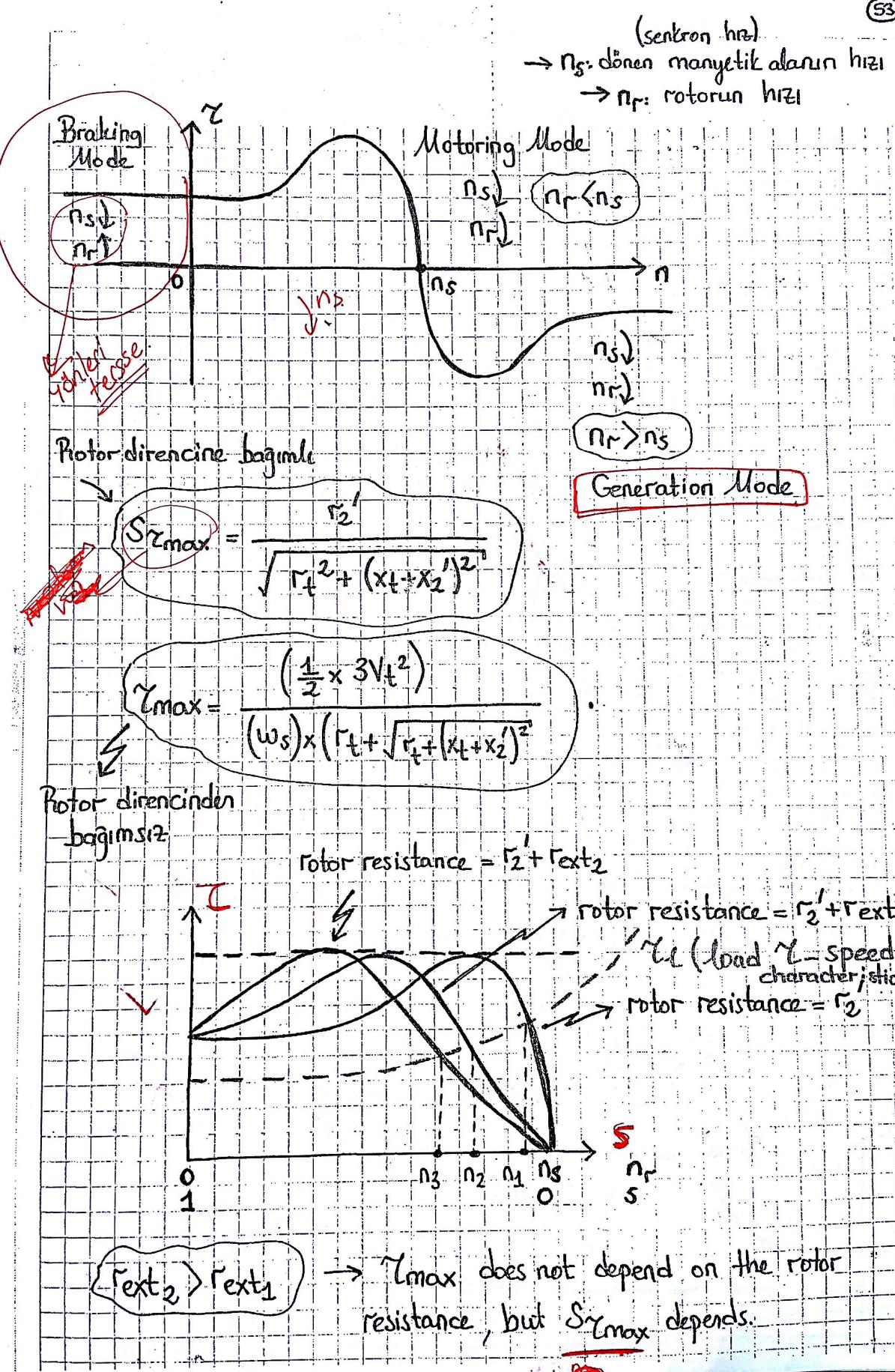d) $\eta = \frac{37300}{42400} \times 100 = 88\% = \frac{P_{out,net} \times 100}{P_e}$



$$\gamma = \frac{1}{w_s} \times \frac{3 \times \frac{1}{2} V_t^2}{\left(\frac{r_2 + r_2'}{s}\right)^2 + (x_t + x_2')^2} \times \frac{r_2'}{s}$$

$$\gamma \propto V_t^2$$

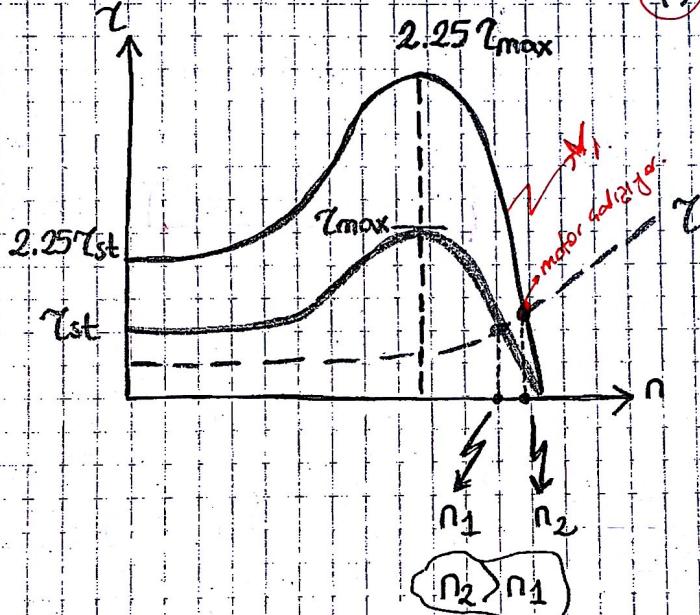

(i) * Speed control of an IM by varying the applied voltage

* The generated torque is proportional with V_t^2

$$V_{t_1} = 1.5 V_t$$


(ii) * The speed of motor can be adjusted by varying the rotor resistance

(iii) * The speed control by varying synchronous speed, n_s .

$$n_s = \frac{120f}{P} \rightarrow \text{pole}$$

$$f_2 = 2f_1$$


$$P_2 = 2P_1$$

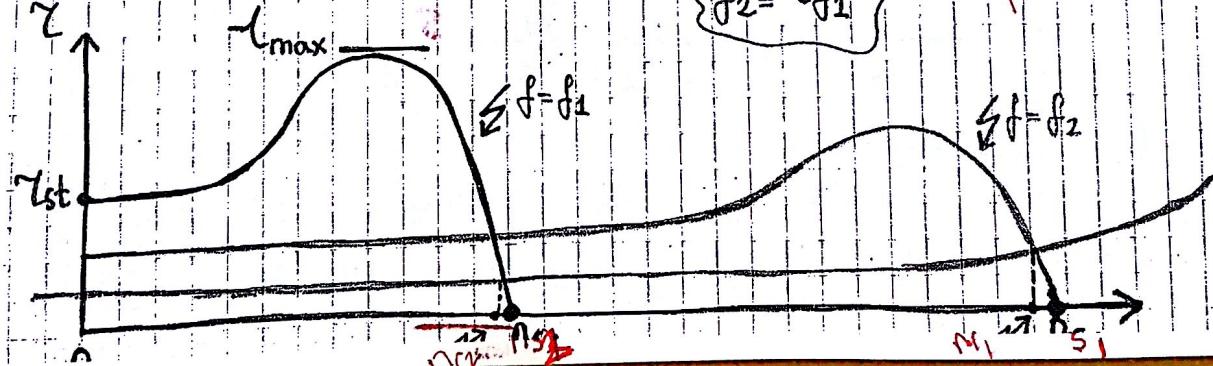

$$5 \text{ h-a} \quad n_s = \frac{2f}{P} \quad n_s = \frac{2 \times 60 \times 120}{P} \quad \text{deur deur}$$

$$a) \quad s = \frac{n_s - n_r}{n_s}$$
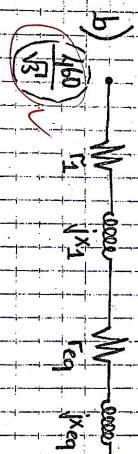
$$\frac{2.2}{100} = \frac{1800 - n_r}{1800} \Rightarrow n_r = 1760 \text{ rpm}$$



$$r_{eq} + jx_{eq} = (j\omega_m) \parallel \left[\frac{0.332}{0.022} + j0.464 \right] = 12.94 \angle 31.1^\circ$$

$$0.332 + \frac{0.332(1-s)}{s} = \frac{0.332}{s}$$

$$r_{eq} = 12.94 \cos(31.1^\circ)$$

$$x_{eq} = 12.94 \sin(31.1^\circ)$$

$$I_1 = \frac{460}{\sqrt{3}} \angle 0^\circ = 266 \angle 0^\circ \text{ Voltaj}$$

$$0.644 + j1.106 + 12.94 \cos(31.1^\circ) + j12.94 \sin(31.1^\circ)$$

$$= 18.88 \angle -33.6^\circ \text{ A}$$

end of the line

c)

$$\boxed{\text{PF} = \cos \phi < 1}$$

$$\phi = 33.6^\circ \text{ (Alum genize) (lagging)}$$

$$\text{PF} = \cos(33.6^\circ) = 0.833$$

elba


(55)

$\frac{f_2}{2\omega}$
long

d) $P_{m,int} \text{ or } P_{conv} = 3 \times \frac{I_2'(1-s)}{s} \left(\frac{f_2'}{f_2} \right)^2$

$(f_2' = 0.332)$

$(s = 0.022)$

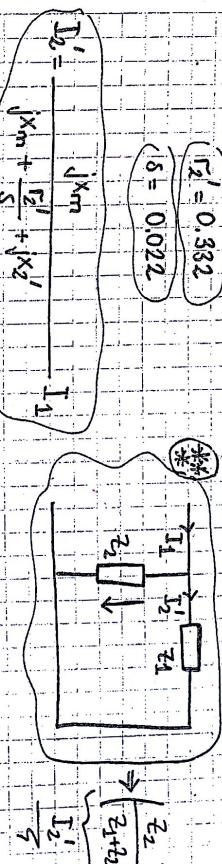

$I_2' = \frac{\sqrt{x_m} + \frac{f_2'}{s} + jx_2'}{I_1}$

$I_2' = \frac{j26.3}{j26.3 + \frac{0.332}{0.022} + j0.464} * 18.88$

Haffaya

Carsompa

Quiz

11 May 5 2014

$P_{out} = (P_{m,int} \text{ or } P_{conv}) - P_{rotational}$

$= 11585 - 1100 \Rightarrow P_{out} = 10485 \text{ W}$

e) $(P = \gamma \omega r)$

$P_{out} = (P_{m,int} \text{ or } P_{conv}) - P_{rotational}$

$= 11585 - 1100 \Rightarrow P_{out} = 10485 \text{ W}$

$P_{m,int} = \gamma_{m,int} \omega r$

$11585 = \gamma_{m,int} \left(\frac{14760}{60} 2\pi \right)$

$(\gamma_{m,int} = 62.8 \text{ N.m})$

$T_{out} = T_{load} = \frac{P_{out}}{\omega r} = \frac{10485}{\left(\frac{14760}{60} \times 2\pi \right)} = (56.9 \text{ N.m})$

f) efficiency $\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{10485}{83.7} \times 100 = 83.7\%$

$P_{in} = \sqrt{3} V_{line-to-line} I_L \cos \phi$

$P_{in} = \sqrt{3} \times 460 \times 18.88 \cos(33.6) = 12530 \text{ W}$